



Review Test Submission: Midterm 3

User	Nafiz Imtiaz
Course	Spring 2021 TTU Modern Digital System Design (ECE-2372-D01)
Test	Midterm 3
Started	4/26/21 7:29 PM
Submitted	4/26/21 8:14 PM
Due Date	4/26/21 11:59 PM
Status	Completed
Attempt Score	92 out of 104 points
Time Elapsed	45 minutes out of 50 minutes
Results Displayed	All Answers, Submitted Answers, Correct Answers

Question 1

4 out of 4 points

What will the next state of a register be if $C = 0$ and $L = 1$

Selected Answer: ☒ C. D

Answers: A. Undefined

B. Q


☒ C. D

D. Zeros

 Question 2

4 out of 4 points

How many D Flip-Flops are present in the given register?



Selected Answer: ☒ A. 16

Answers: ☒ A. 16

B. 8

C. 4

D. 32

Question 3

4 out of 4 points

What will the state of a Set'-Reset' Latch be at the end of the following sequence of inputs?

S	R
1	1
1	0
1	1
0	1
0	0
0	0
1	0
0	1
0	0

Selected Answer: ☒ B. INVALID

Answers:

A. UNDEFINED

☒ B. INVALID

C. SET

D. RESET

Question 4

4 out of 4 points

For a **Parallel Adder with Accumulator**, what will be the output at the end of the following sequence of inputs?

D	RST
1	1
3	0
2	0
5	0
7	1
4	0
2	0

Selected Answer: ☒ C. 6

Answers:

A. 18

B. 24

☒ C. 6

D. 13

Question 5

4 out of 4 points

What will the state of a falling edge-triggered J-K Flip-Flop be at the end of the following sequence of inputs?

CLK	J	K
0	1	0

1	0	0
0	0	1
1	0	0
0	0	0
1	1	1
0	0	0
1	0	1
0	1	1

Selected Answer: ☒ A. RESET

Answers:

- ☒ A. RESET
- ☐ B. SET
- ☐ C. UNDEFINED
- ☐ D. INVALID

Question 6

4 out of 4 points

What will the state of a D Latch be at the end of the following sequence of inputs?

G	D
0	0
0	0
1	0
1	1
0	1
0	0
1	0
1	0
0	0

Selected Answer: ☒ B. RESET

Answers:


- ☐ A. INVALID
- ☒ B. RESET
- ☐ C. UNDEFINED
- ☐ D. SET

Question 7

4 out of 4 points

A 4-bit PIPO right shift register is initially loaded with the state $Q = 4'd13$. What will the the output Q be at the end of the following sequence of inputs?


SI	SHIFT	LOAD	D
0	1	0	4'd7
0	1	1	4'd4
1	0	1	4'd10
1	1	0	4'd5
1	0	0	4'd8
1	1	0	4'd9

Selected Answer:  D. 4'b1110

Answers: A. 4'b1010

B. 4'b1101


C. 4'b0111

 D. 4'b1110

 Question 8

4 out of 4 points

For the given state graph, what will the next-state and output be if the present state is S3 and the input is 11?



Selected Answer: ☒ B. S0, 01

Answers:

- A. S0, 00
- ☒ B. S0, 01
- C. S2, 00
- D. S1, 01

Question 9

4 out of 4 points

What is the Next-State equation for flip-flop B in a 2-bit arbitrary sequence binary counter, with enable, with the given sequence?

Q_A^+	Q_B^+
1	0
0	0
1	1
0	1

Selected Answer: ☒ B. $E'B + AB + EA'B$

Answers:


- A. $EA' + EB + A'B'$

- ☒ B. $E'B + AB + EA'B$
- C. $E'AB + A'B' + E'B'$
- D. $E'A'B + EAB + EA'$

Question 10

0 out of 4 points

What type of sequential circuit is shown?

 Selected Answer: ☒ A. Moore

Answers:

- A. Moore
- B. Boolean
- ☒ C. Mealy
- D. Flip-Flop


Question 11

4 out of 4 points


What will the state of a rising edge-triggered S-R Flip-Flop be at the end of the following sequence of inputs?

CLK	S	R
0	1	0
1	0	0
0	0	0

1	0	1
0	0	1
1	1	1
0	0	0
1	1	0
0	1	0

Selected Answer:  B. RESET


Answers:

- A. INVALID
-  B. RESET
- C. UNDEFINED
- D. SET


Question 12

4 out of 4 points

What is the dominant input signal for the AND-gate?

Selected Answer:  B. 0

Answers:


- A. X
-  B. 0
- C. 1
- D. Z

Question 13

4 out of 4 points

What will be the state of a Set-Reset Latch at the end of the following sequence of inputs?

S	R
1	0
0	0
1	0
0	1
0	0
1	0
0	0

Selected Answer:  D. SET

Answers:

- A. RESET
- B. INVALID
- C. UNDEFINED
- ☒ D. SET

Question 14

4 out of 4 points

What will the state of a Gated Set-Reset Latch be at the end of the following sequence of inputs?

G	S	R
0	0	0
0	1	0
1	0	1
1	0	0
0	1	0
1	1	1
1	1	0
0	0	0
0	0	1

Selected Answer: ☒ D. SET

Answers:

- A. UNDEFINED
- B. RESET
- C. INVALID
- ☒ D. SET

Question 15

4 out of 4 points

Assuming that the flip-flop is initially in the RESET state, what will be the state of a falling edge-triggered T Flip Flop be at the end of the following sequence of inputs?

CLK	T

0	0
1	0
0	1
1	1
0	1
1	0
0	0
1	1
0	0

Selected Answer: ☒ B. RESET

Answers:

- ☐ A. INVALID
- ☒ B. RESET
- ☐ C. SET
- ☐ D. UNDEFINED

Question 16

4 out of 4 points

For the given state table, what will the next-state and output be if the present-state is S_2 and the input $X_1X_2 = 10$?

Present State	Next State				Present Output (Z_1Z_2)			
	$X_1X_2 = 00$	01	10	11	$X_1X_2 = 00$	01	10	11
S_0	S_3	S_2	S_1	S_0	00	10	11	01
S_1	S_0	S_1	S_2	S_3	10	10	11	11
S_2	S_3	S_0	S_1	S_1	00	10	11	01
S_3	S_2	S_2	S_1	S_0	00	00	01	01

Selected Answer: ☒ D. $S_1, 11$

Answers:

- ☐ A. $S_3, 11$
- ☐ B. $S_0, 10$
- ☐ C. $S_1, 01$
- ☒ D. $S_1, 11$

Question 17

4 out of 4 points

If a Mealy circuit has a 3-bit input, 10 states, and a 2-bit output, then it will be defined by how many equations of how many variables?

Selected Answer: ☒ B. 6 equations of 7 variables

Answers: A. 4 equations of 7 variables

☒ B. 6 equations of 7 variables

C. 7 equations of 4 variables

D. 2 equations of 3 variables

Question 18

4 out of 4 points

A 3-bit synchronous binary counter is initially loaded with 3'd6. What will the state of the counter be at the end of the following sequence of inputs?

COUNT	RESET
1	1
1	0
0	0
1	0
1	0
1	0

Selected Answer: ☒ B. 3'b100

Answers: A. 3.b011

☒ B. 3'b100

C. 3'b111

D. 3'b101

Question 19

4 out of 4 points

For the given transition table, what is the Next State Equation for Flip-Flop B?

Present State (AB)	Next State (A^+B^+)		Output (F)	
	$X = 0$	$X = 1$	$X = 0$	$X = 1$
00	00	01	0	1
01	01	11	1	0
11	11	00	0	1
10	10	01	0	1

Selected Answer: ☒ C. $X'B + A'B + XB'$

Answers:

A. $X'B + XA'B + AB'$

B. $XA'B' + AB' + XB'$


☒ C. $X'B + A'B + XB'$

D. $X'A' + X'B + AB'$

 Question 20

4 out of 4 points

For the given sequential circuit, What will the output sequence be for the input sequence $X = \{0, 1, 1, 0, 1\}$



Selected Answer: ☒ B. $Z = \{0, 1, 0, 0, 1\}$

Answers:

A. $Z = \{0, 1, 0, 0, 0\}$

- ☒ B. $Z = \{0, 1, 0, 0, 1\}$
- C. $Z = \{0, 1, 1, 0, 1\}$
- D. $Z = \{0, 1, 0, 1, 0\}$

Question 21

4 out of 4 points

For the given register circuit, how will the command **LOAD Y B**; effect the control inputs **S** and **ADDR**?

Selected Answer: ☒ D. $S = 1, ADDR = 0$

- Answers:
- A. $S = 0, ADDR = 0$
- B. $S = 1, ADDR = 1$
- C. $S = 0, ADDR = 1$
- ☒ D. $S = 1, ADDR = 0$

Question 22

4 out of 4 points

If a Moore circuit has a 3-bit input, 17 states, and a 2-bit output. How many output equations of how many variables will be needed?


Selected Answer: ☒ D. 2 equations of 5 variables


- Answers:
- A. 2 equations of 4 variables
- B. 7 equations of 8 variables
- C. 4 equations of 5 variables
- ☒ D. 2 equations of 5 variables

 Question 23


4 out of 4 points

What is the sequence X that is shown in the following timing chart?



Selected Answer:  B. $X = \{0, 1, 0, 0, 0, 1, 1, 1\}$

Answers: A. $X = \{0, 0, 1, 0, 1, 1, 1, 0\}$

 B. $X = \{0, 1, 0, 0, 0, 1, 1, 1\}$


C. $X = \{0, 1, 0, 1, 1, 1, 0, 0\}$

D. $X = \{0, 0, 1, 1, 0, 1, 0, 1\}$


Question 24

0 out of 4 points

Which of the following RTL commands defines a 5-bit internal register?

Selected Answer:  A. output reg [4:0] myReg;

Answers: A. output reg [4:0] myReg;

 B. reg [4:0] myReg;

C. output reg [5:0] myReg;


D. output [4:0] myReg;

Question 25

4 out of 4 points


What will the state of a falling edge-triggered D Flip-Flop be after the following sequence of inputs?

CLK	D
0	0
1	1
0	1
0	1
1	0
0	1
1	0
1	0
0	1

Selected Answer:  C. RESET

Answers: A. UNDEFINED

B. SET

 C. RESET

D. INVALID

Question 26

Which of the following RTL commands will cause the logic instructions to trigger on both the rising and falling edges of B?

Selected Answer:  always@(CLK)

Answers:  always@(B)

always@(CLK)

always@(posedge & negedge B)

always@(posedge CLK | negedge CLK)

Thursday, April 29, 2021 4:05:57 PM CDT

← OK