 


ECE 2372 | Modern Digital System Design | Texas Tech University

# Latches



# Lecture Overview

1. Combinational vs Sequential Logic
2. Dominant Inputs
3. Set-Reset Latch
4. Set'-Reset' Latch
5. Gated Set-Reset Latch

# Combinational vs Sequential Logic

**Latches** | Modern Digital System Design

# Combinational vs Sequential Logic

So far, we've been working with **combinational logic**.



# Combinational vs Sequential Logic

Sequential Logic builds on this model by adding **State**.



# Combinational vs Sequential Logic



To make this work, we need a logic circuit that **maintain the state**.  
Even if the input signal changes.

# Dominant Input Signals

**Latches** | Modern Digital System Design

# Dominant Input Signals

The logic gates AND, NAND, OR, and NOR have truth tables with a similar pattern.

| A | B | AND |
|---|---|-----|
| 0 | 0 | 0   |
| 0 | 1 | 0   |
| 1 | 0 | 0   |
| 1 | 1 | 1   |

| A | B | OR |
|---|---|----|
| 0 | 0 | 0  |
| 0 | 1 | 1  |
| 1 | 0 | 1  |
| 1 | 1 | 1  |



# Dominant Input Signals

The **dominant input signal**, either 1 or 0, is the signal which drives the logic gate to a specific state if it appears anywhere in the input.

| A | B | AND |
|---|---|-----|
| 0 | 0 | 0   |
| 0 | 1 | 0   |
| 1 | 0 | 0   |
| 1 | 1 | 1   |

For the AND-gate, notice that a 0 anywhere drives the gate to 0.

# Dominant Input Signals

The **dominant input signal**, either 1 or 0, is the signal which drives the logic gate to a specific state if it appears anywhere in the input.

| A | B | AND |
|---|---|-----|
| 0 | 0 | 0   |
| 0 | 1 | 0   |
| 1 | 0 | 0   |
| 1 | 1 | 1   |

For the AND-gate, notice that a 0 anywhere drives the gate to 0.  
**0 is the dominant signal for an AND-gate.**

# Dominant Input Signals

| A | B | OR |
|---|---|----|
| 0 | 0 | 0  |
| 0 | 1 | 1  |
| 1 | 0 | 1  |
| 1 | 1 | 1  |


For the OR-gate, notice that a 1 anywhere drives the gate to 1.

# Dominant Input Signals

| A | B | OR |
|---|---|----|
| 0 | 0 | 0  |
| 0 | 1 | 1  |
| 1 | 0 | 1  |
| 1 | 1 | 1  |

For the OR-gate, notice that a 1 anywhere drives the gate to 1.  
1 is the dominant input signal for the OR-gate.

# What questions do you have?

 

# EXAM PROBLEM | Dominant Input Signals

What is the dominant input signal for the NOR-gate?

- A. 1
- B. 0
- C. The NOR-gate does not have a dominant input signal.

# EXAM PROBLEM | Dominant Input Signals

What is the dominant input signal for the NOR-gate?

A. 1

~~B. 0~~

~~C. The NOR-gate does not have a dominant input signal.~~


| A | B | NOR |
|---|---|-----|
| 0 | 0 | 1   |
| 0 | 1 | 0   |
| 1 | 0 | 0   |
| 1 | 1 | 0   |

# Set-Reset Latch

**Latches** | Modern Digital System Design




# Set-Reset Latch

 

By convention, we use  $Q$  to represent the state of the latch.

# Set-Reset Latch

 

By convention, we use  $Q$  to represent the state of the latch.

$Q = 1$  (SET),  $Q = 0$  (RESET)


# Set-Reset Latch

1 | 0



# Set-Reset Latch


1 | 0

 

Since NOR is dominated by 1, we must have a 0 on the output of the bottom NOR-gate.

# Set-Reset Latch


1 | 0

 

The 1 from Q will continue to dominate the bottom NOR-gate. Our **SET** state is maintained, even with all 0's on the input.

# Set-Reset Latch


1 | 0

 

Since NOR is dominated by 1, we must have a 0 on the output of the top NOR-gate.

# Set-Reset Latch


1 | 0

 

The 1 from  $Q'$  will continue to dominate the top NOR-gate.  
Our **RESET** state is maintained, even with all 0's on the input.

# Set-Reset Latch

1 | 0

 


By applying the dominant input to both inputs, both NOR-gates are forced to 0. Since, Q and Q' cannot both be 0, this is an **INVALID** state.



# Set-Reset Latch
 
## Recap

- When both inputs are non-dominant, the state will not change.
- Apply a dominant input to one input to SET/RESET the state.
- Applying the dominant input on both inputs yields an INVALID STATE



# What questions do you have?



# EXAM PROBLEM | Set-Reset Latch

What will be the state of a Set-Reset Latch at the end of the following sequence of inputs?

- A. SET
- B. RESET
- C. INVALID

| S | R |
|---|---|
| 1 | 0 |
| 0 | 0 |
| 0 | 1 |
| 1 | 1 |
| 0 | 0 |
| 1 | 0 |
| 0 | 0 |

# EXAM PROBLEM | Set-Reset Latch

What will be the state of a Set-Reset Latch at the end of the following sequence of inputs?

A. SET

~~B. RESET~~

~~C. INVALID~~


| S | R |         |
|---|---|---------|
| 1 | 0 | SET     |
| 0 | 0 | SET     |
| 0 | 1 | RESET   |
| 1 | 1 | INVALID |
| 0 | 0 | INVALID |
| 1 | 0 | SET     |
| 0 | 0 | SET     |

# Set'-Reset' Latch


**Latches** | Modern Digital System Design
 
# Set'-Reset' Latch

The Set'-Reset' Latch provides an alternate implementation which we'll use for more complex designs.




# Set'-Reset' Latch

 

What is the dominant input for the Set'-Reset' Latch?

# Set'-Reset' Latch

 


What is the dominant input for the Set'-Reset' Latch?

0 is the dominant input for the NAND-gate




# Set'-Reset' Latch

1 | 0

 

# Set'-Reset' Latch


1 | 0

 

Since 0 is the dominant input, the top NAND-gate will be forced to 1.

# Set'-Reset' Latch


1 | 0

 

The 0 from Q' will continue to dominate the top NAND-gate. Our **SET** state is maintained, even with all 1's on the input.

# Set'-Reset' Latch


1 | 0

 

Since 0 is the dominant input, the bottom NAND-gate will be forced to 1.

# Set'-Reset' Latch


1 | 0

 

The 0 from Q will continue to dominate the BOTTOM NAND-gate. Our **RESET** state is maintained, even with all 1's on the input.

# Set'-Reset' Latch


1 | 0

 

By applying the dominant input to both inputs, both NAND-gates are forced to 1. Since, Q and Q' cannot both be 1, this is an **INVALID** state.
 
# Set'-Reset' Latch

- Same behavior as the Set-Reset Latch except 0 is the dominant input



# What questions do you have?





# EXAM QUESTION | Set'-Reset' Latch

What will be the state of a Set'-Reset' Latch at the end of the following sequence of inputs?

- A. SET
- B. RESET
- C. INVALID

| S | R |
|---|---|
| 1 | 0 |
| 1 | 1 |
| 0 | 1 |
| 1 | 1 |
| 1 | 1 |
| 1 | 0 |
| 1 | 1 |

# EXAM QUESTION | Set'-Reset' Latch

What will be the state of a Set'-Reset' Latch at the end of the following sequence of inputs?

~~A. SET~~

B. RESET

~~C. INVALID~~

| S | R |
|---|---|
| 1 | 0 |
| 1 | 1 |
| 0 | 1 |
| 1 | 1 |
| 1 | 1 |
| 1 | 0 |
| 1 | 1 |

RESET

RESET

SET

SET

SET

RESET


RESET

# Gated Set-Reset Latch

**Latches** | Modern Digital System Design

 
# Gated Set-Reset Latch

We can expand out Set-Reset Latch to include a **control input** to handle when the state can be set or changed.



# Gated Set-Reset Latch


1 | 0

 

Since 0 is the dominant input, the enable NAND-gates will be forced to 1.

# Gated Set-Reset Latch


1 | 0

 

Since 0 is the dominant input, the enable NAND-gates will be forced to 1. This forces the Set'-Reset' Latch to be in the **NO-CHANGE** state.

# Gated Set-Reset Latch

1 | 0

 

When the enable signal is 1 (non-dominant), the NAND-gate inverts the SET and RESET signals. Now the latch will behave like a SET-RESET Latch.

# What questions do you have?





# EXAM QUESTION | Gated Set-Reset Latch

What will the state of a Gated Set-Reset Latch be at the end of the following sequence of inputs?

- A. SET
- B. RESET
- C. INVALID
- D. UNDEFINED

| G | S | R |
|---|---|---|
| 0 | 0 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |
| 1 | 0 | 0 |
| 0 | 0 | 1 |
| 1 | 1 | 1 |
| 0 | 1 | 0 |

# EXAM QUESTION | Gated Set-Reset Latch

What will the state of a Gated Set-Reset Latch be at the end of the following sequence of inputs?

~~A. SET~~

~~B. RESET~~

C. INVALID

~~D. UNDEFINED~~

| G | S | R |
|---|---|---|
| 0 | 0 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |
| 1 | 0 | 0 |
| 0 | 0 | 1 |
| 1 | 1 | 1 |
| 0 | 1 | 0 |

UNDEFINED

UNDEFINED

SET

SET



SET

INVALID

INVALID

# Lecture Recap

  1. Combinational vs Sequential Logic
2. Dominant Inputs
3. Set-Reset Latch
4. Set'-Reset' Latch
5. Gated Set-Reset Latch



What questions  
do you have?

ECE 2372 | Modern Digital System Design | Texas Tech University

# Latches

