



# Sequential Circuit Analysis

ECE 2372 | Modern Digital System Design | Texas Tech University



# Lecture Overview



Signal Tracing



Timing Charts



Mealy versus Moore Machines



# Signal Tracing

Sequential Circuit Analysis | Modern Digital System Design


# Signal Tracing

- Analyze clocked sequential circuits to find the output sequence resulting from a given input sequence by **tracing 0 and 1 signals** through the circuit.

We've already been doing this.


# Signal Tracing: Procedure

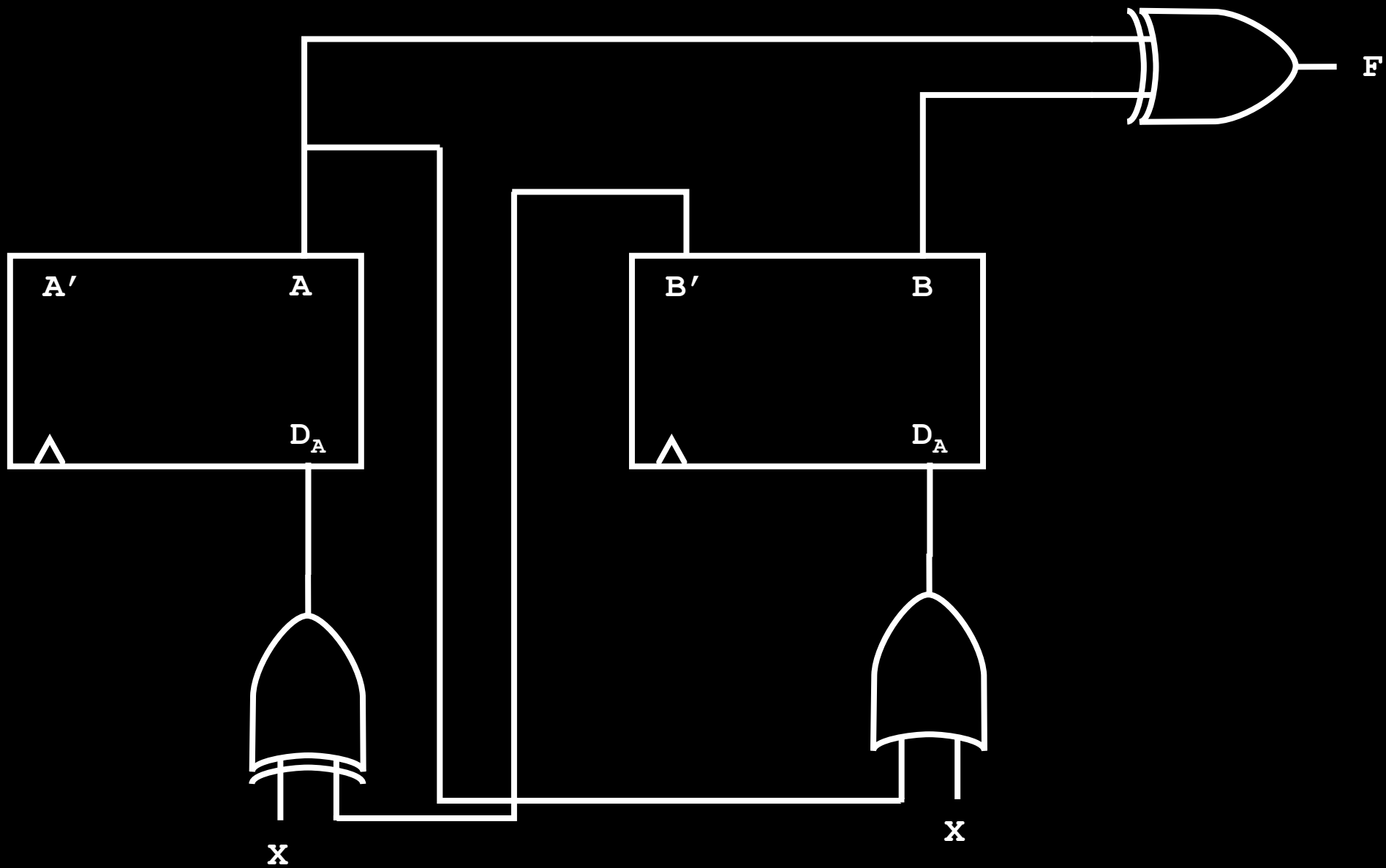1. Assume an initial state of the flip-flops.
  - Assume at rest ( $Q = 0$ ) unless otherwise specified.
2. For the first input in the given sequence, determine the circuit outputs and flip-flop inputs.
3. Determine the new set of flip-flop states after the next active clock edge.
4. Determine the outputs that correspond to the new states.
5. Repeat 2, 3, and 4 for each input in the given sequence.




$X = \{0, 1, 1, 0, 1\}$

*Cycle* = 0

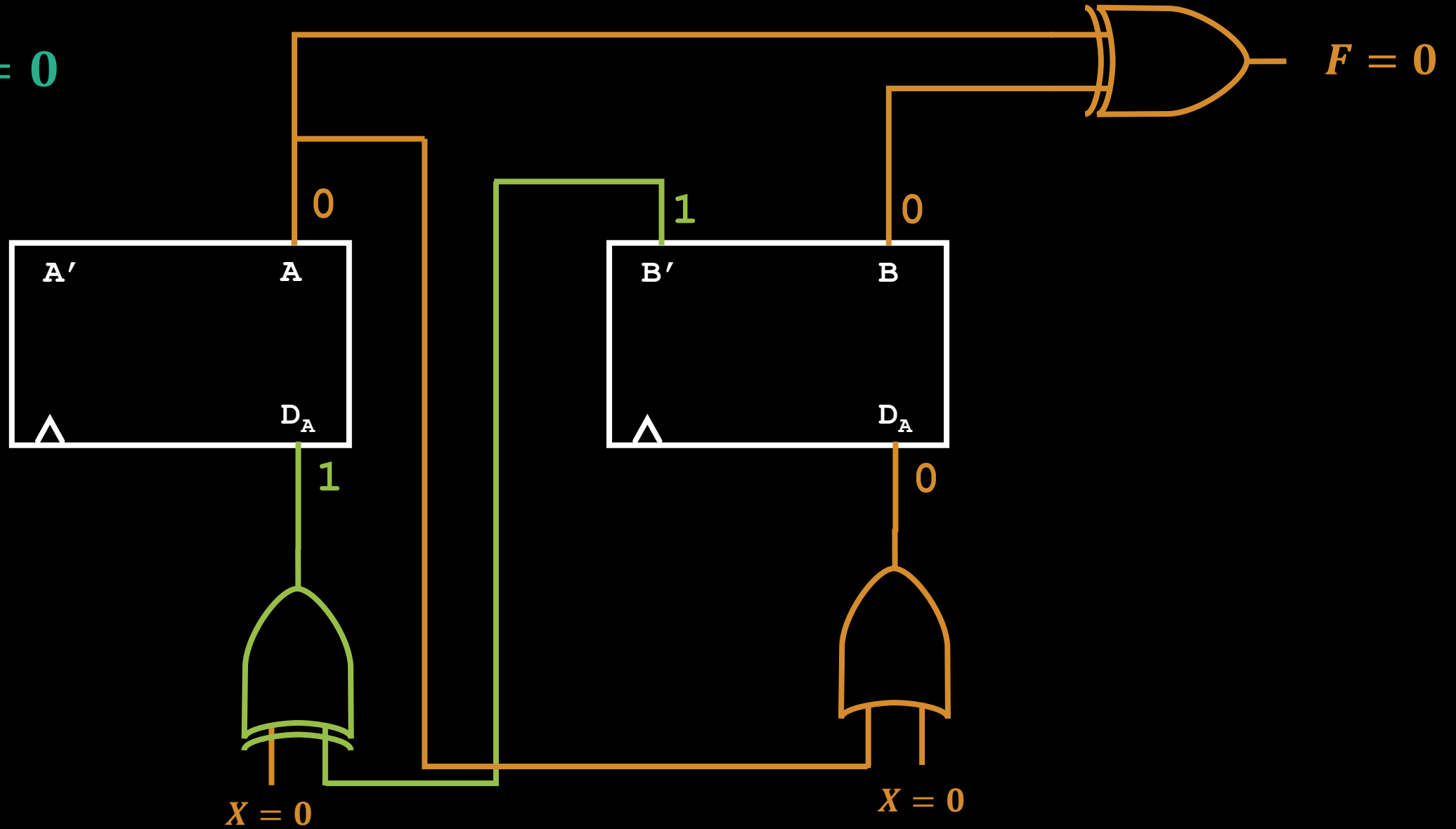

$X = \{1, 1, 0, 1\}$


*Cycle = 1*

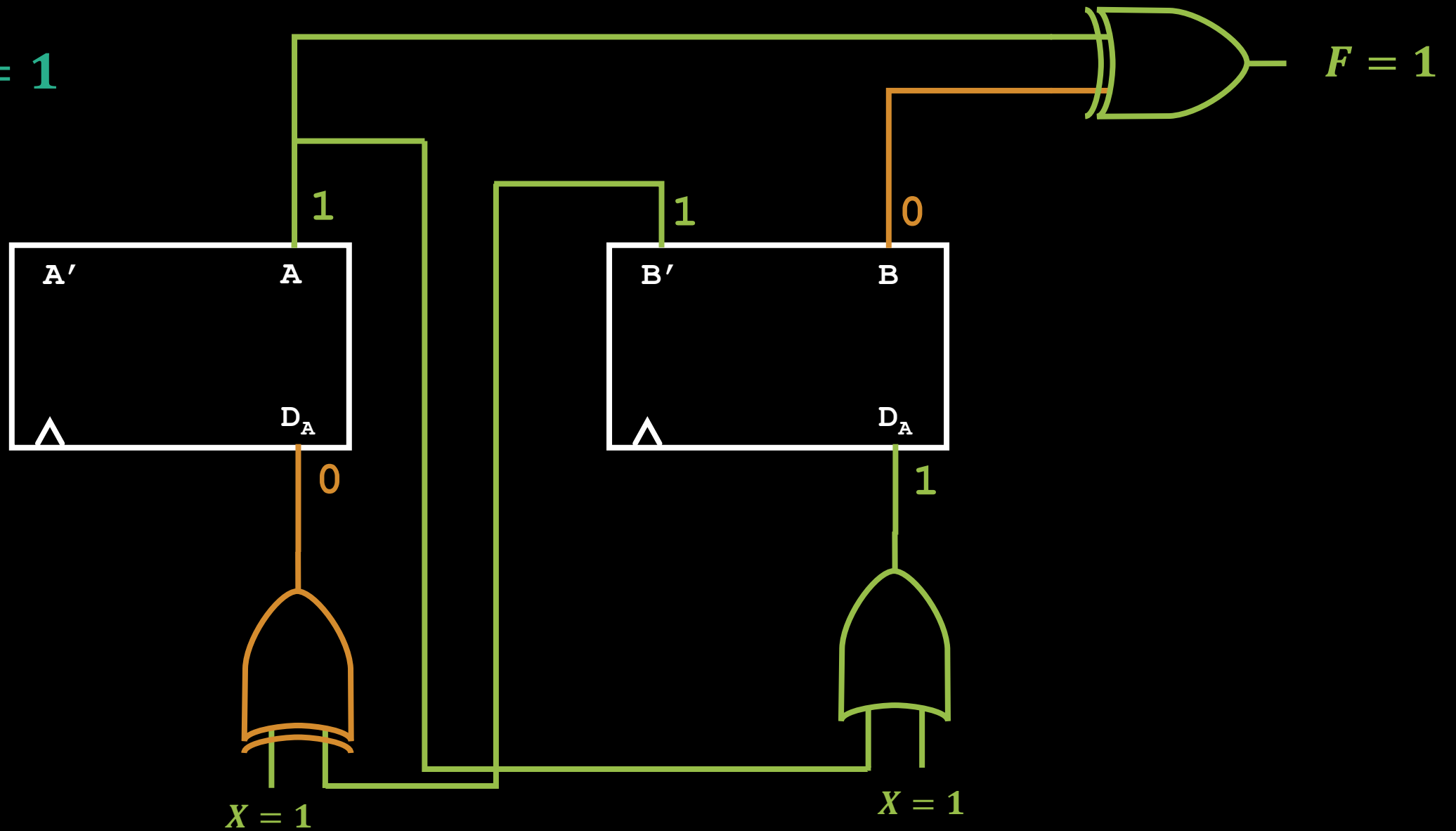




$X = \{1, 0, 1\}$

*Cycle = 2*

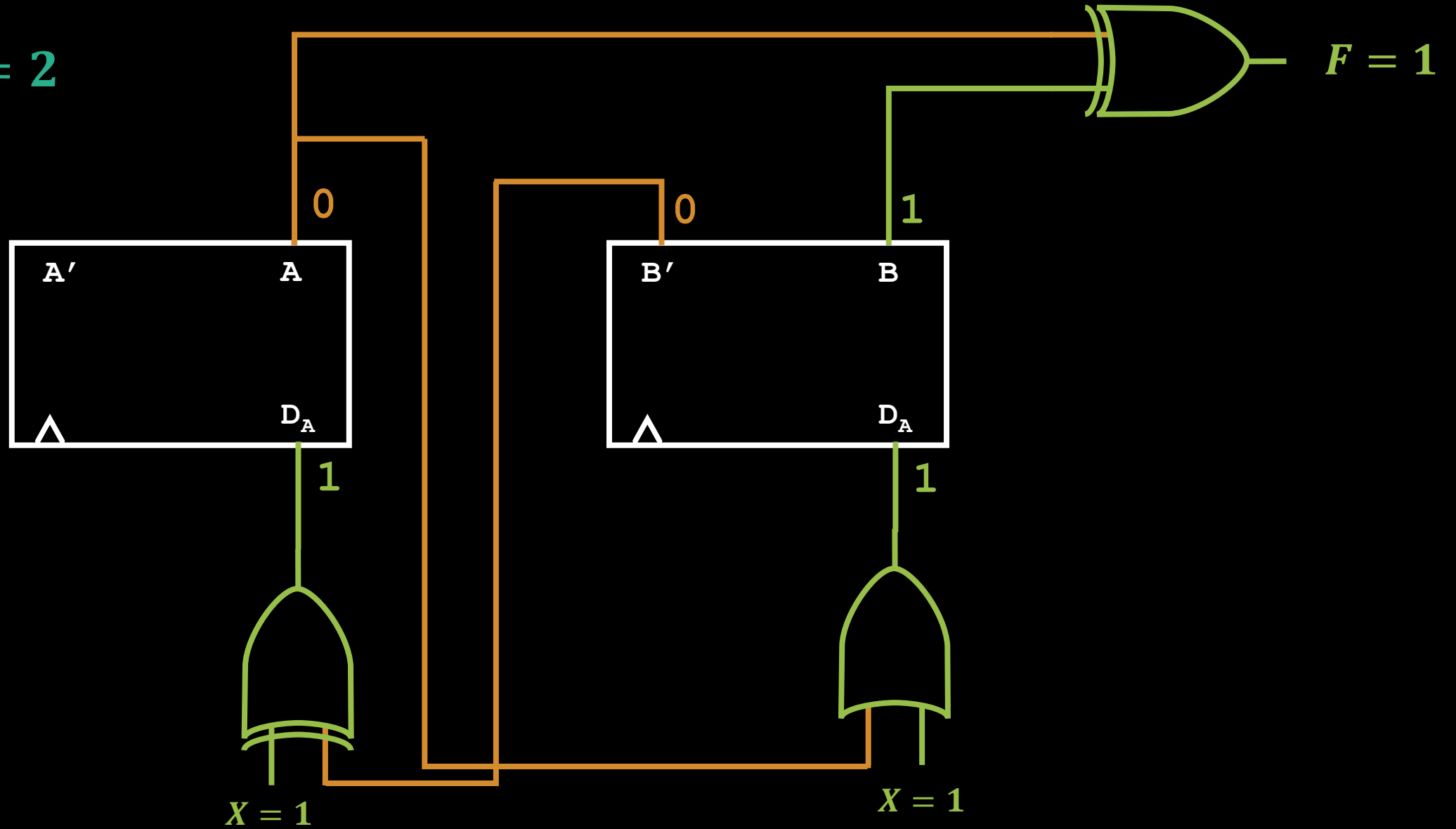


$X = \{1, 0, 1\}$

*Cycle = 3*

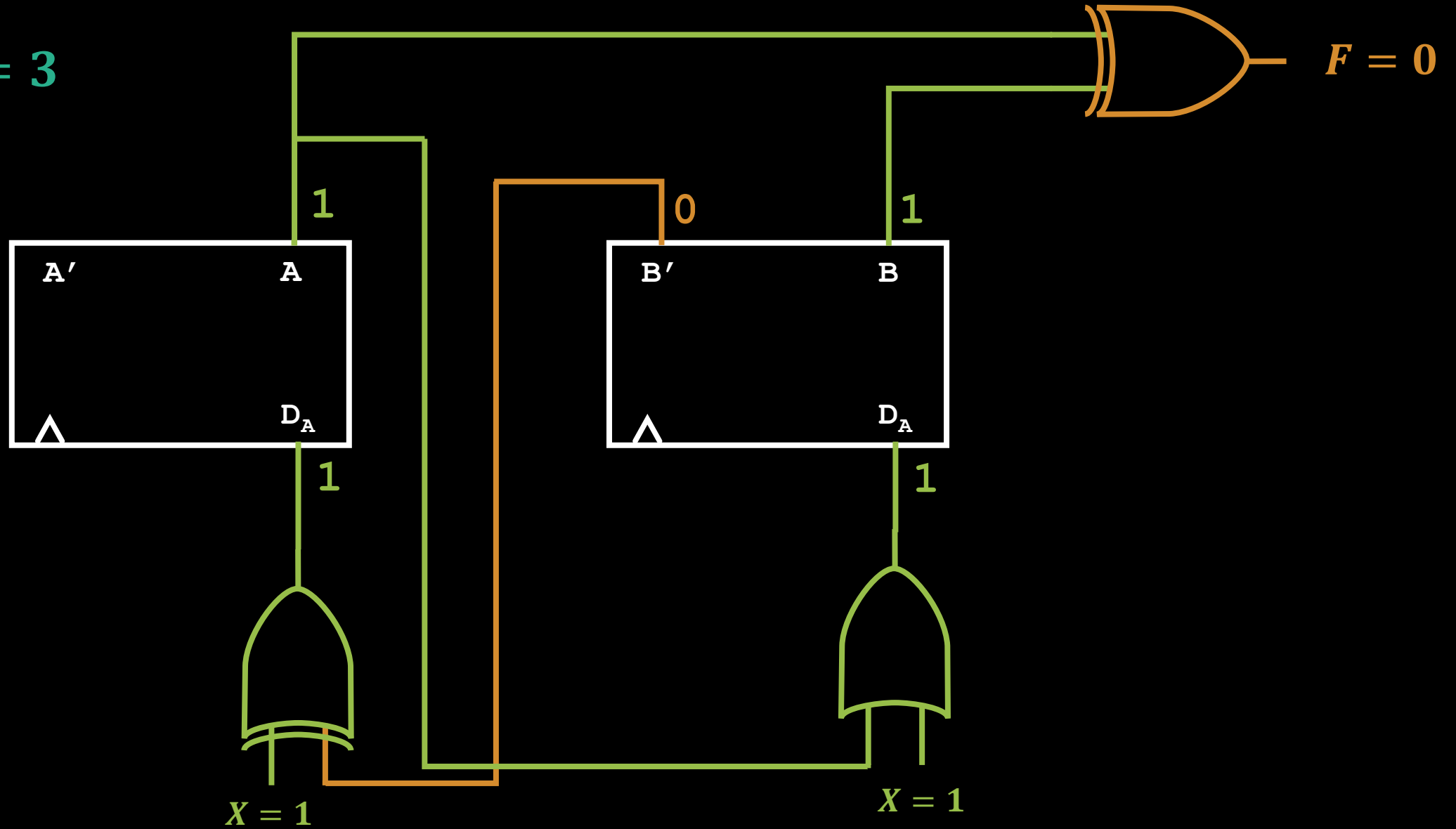


$X = \{0, 1\}$

*Cycle = 4*

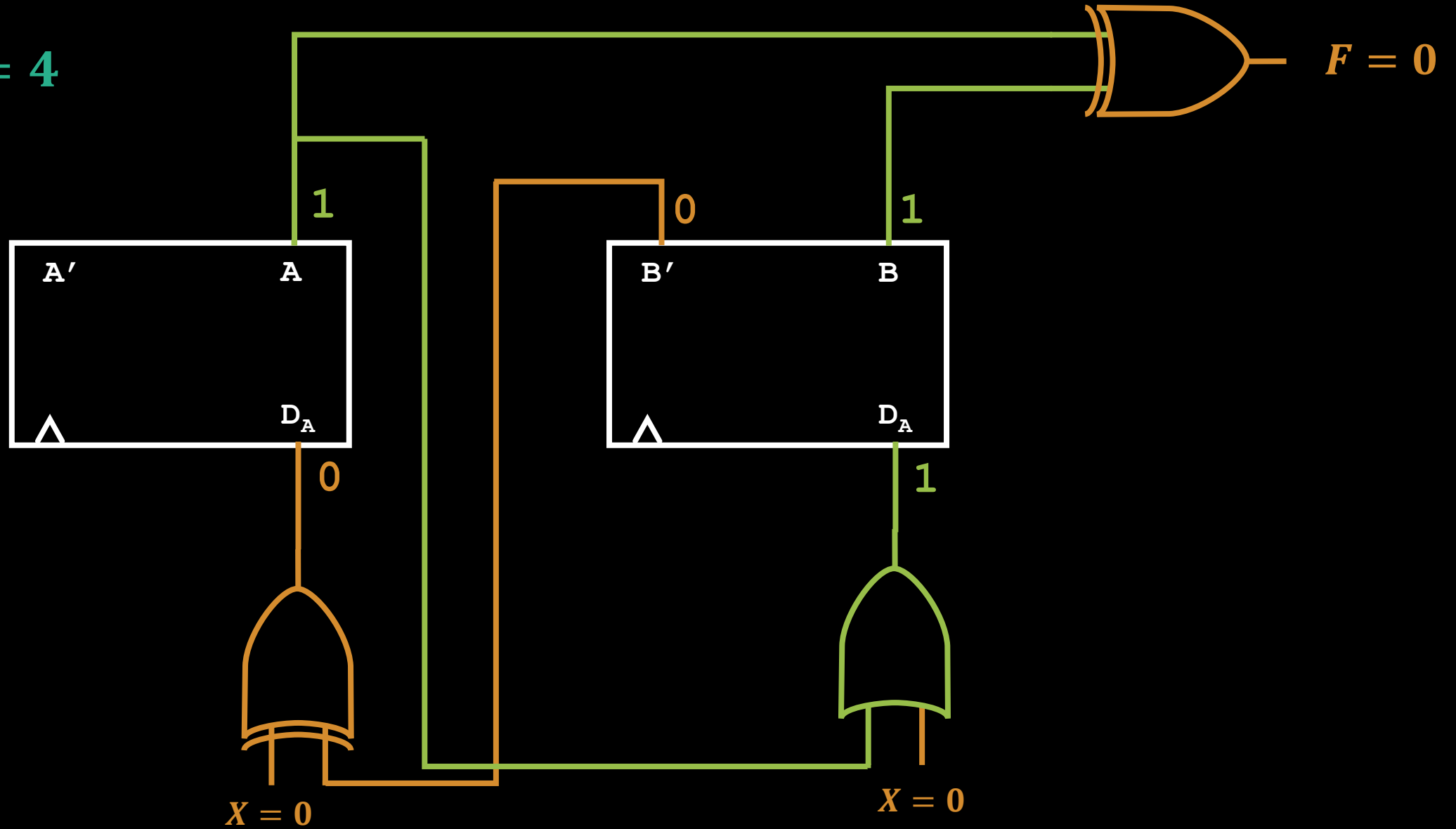

$X = \{1\}$

*Cycle = 5*

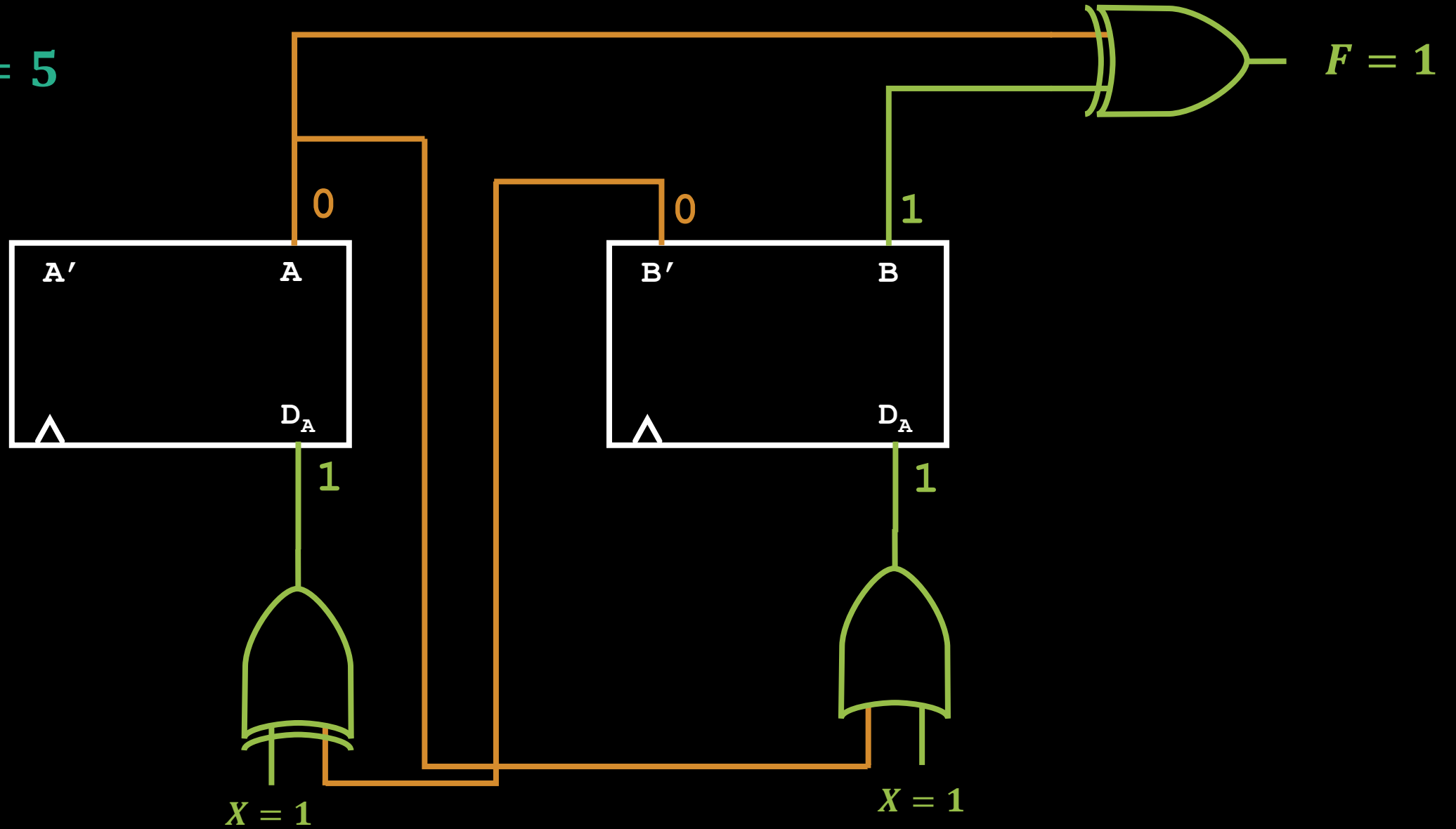

What questions  
do you have?



# EXAM Question: Signal Tracing

For the sequential circuit shown on the next slide, what will the output be at the end of the input sequence?




*A.*  $F = 0$

*B.*  $F = 1$

A.  $F = 0$

B.  $F = 1$




$X = \{1, 0, 1, 0, 1\}$

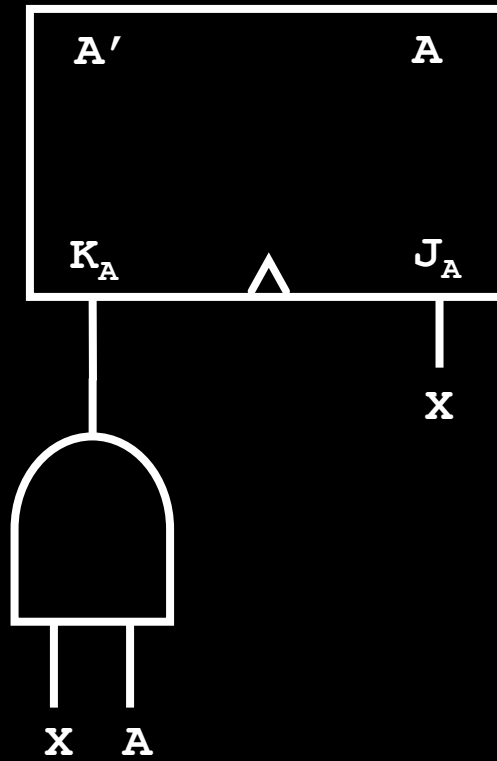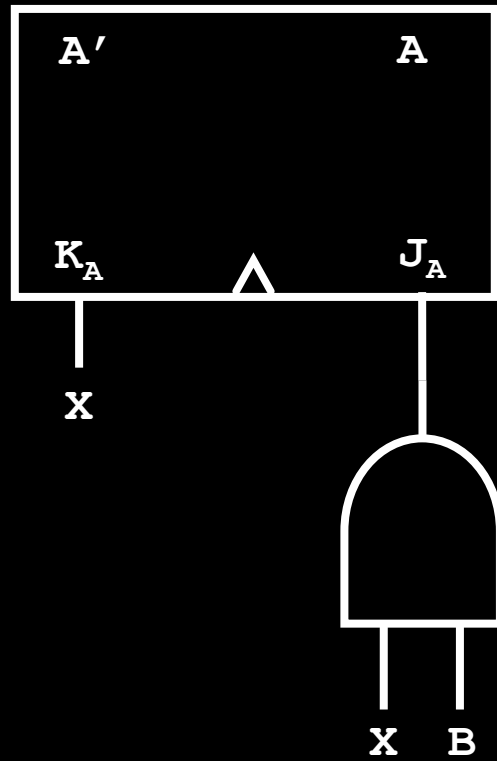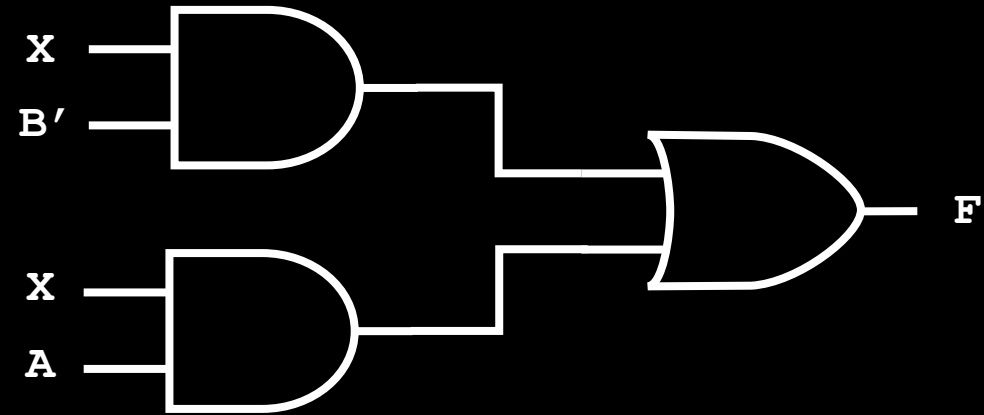

~~A.  $F = 0$~~

B.  $F = 1$

$X = \{1, 0, 1, 0, 1\}$

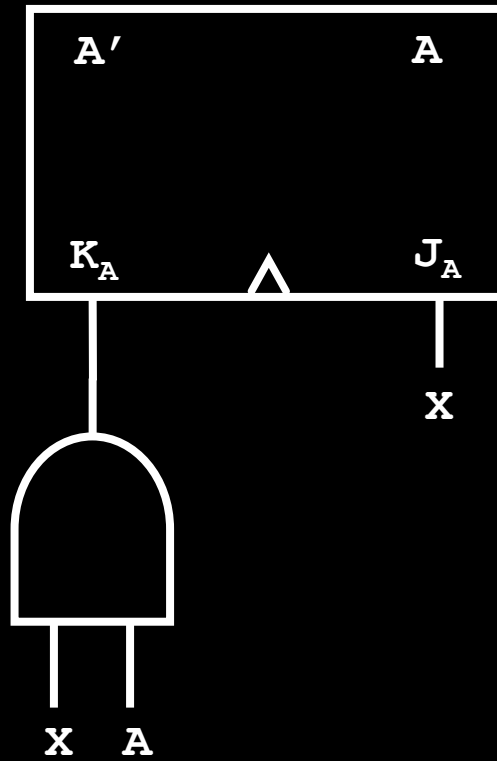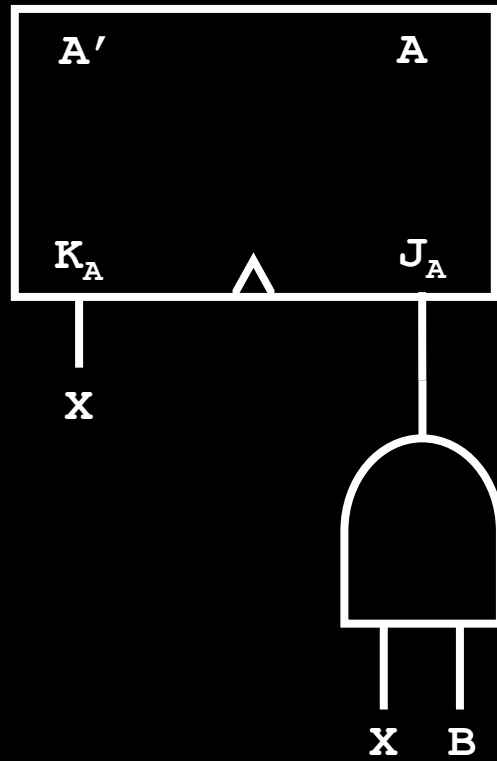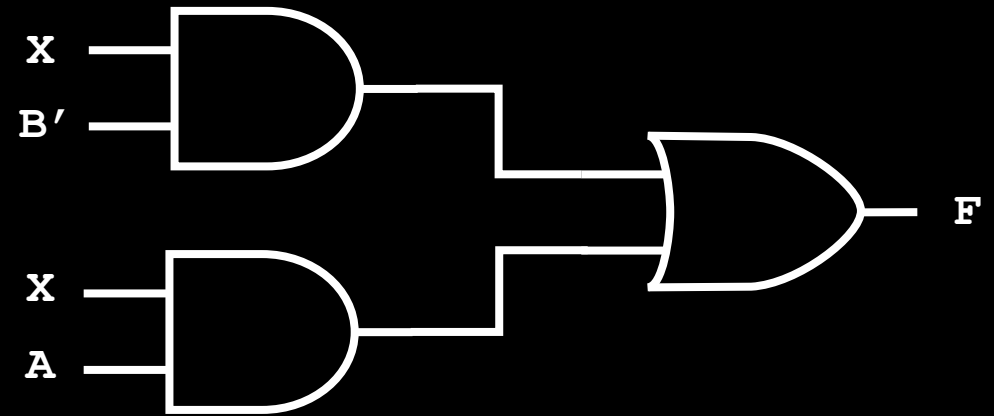






~~A.  $F = 0$~~

B.  $F = 1$

$X = \{1, 0, 1, 0, 1\}$

Cycle = 0

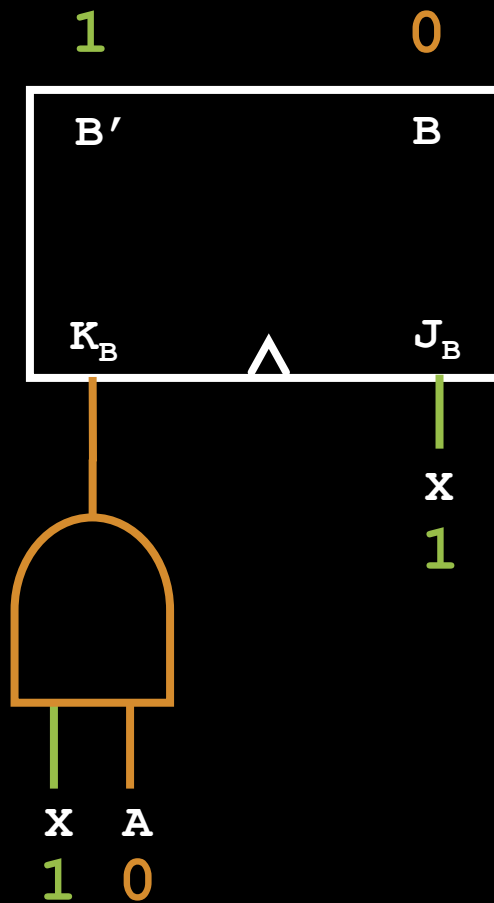
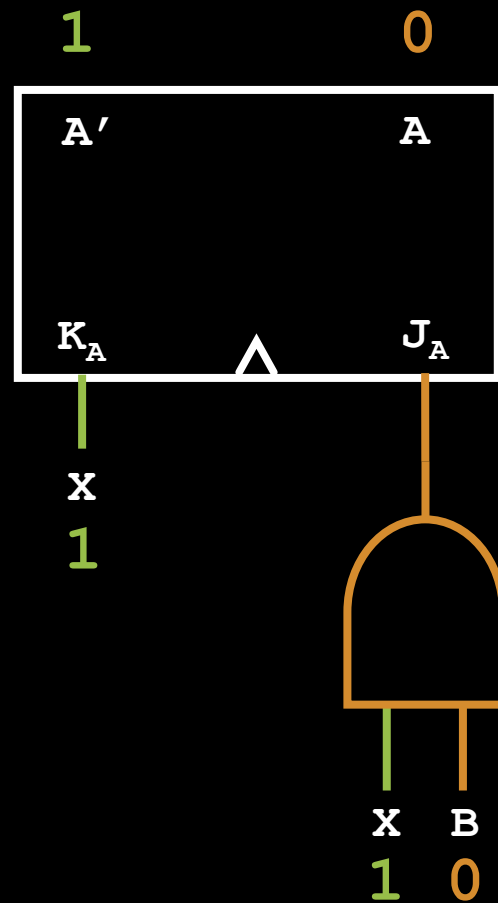
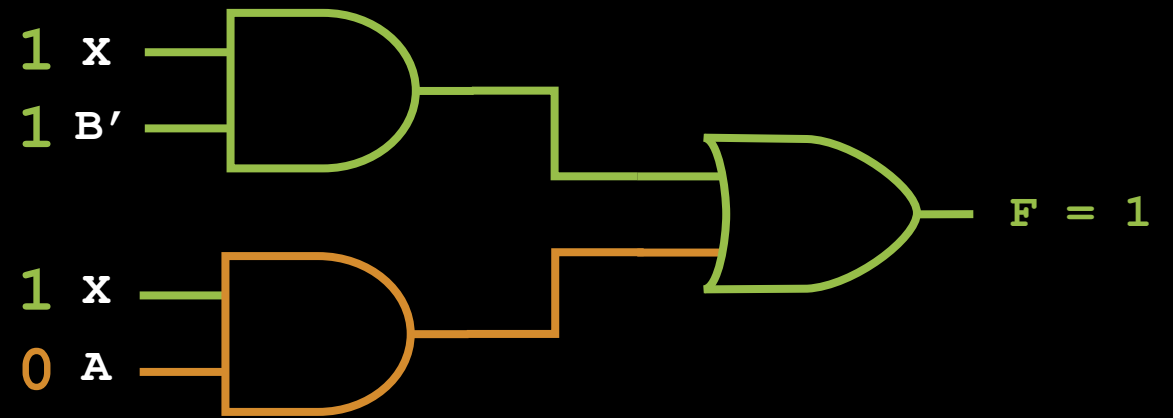


~~A.  $F = 0$~~

B.  $F = 1$

$X = \{0, 1, 0, 1\}$

Cycle = 1

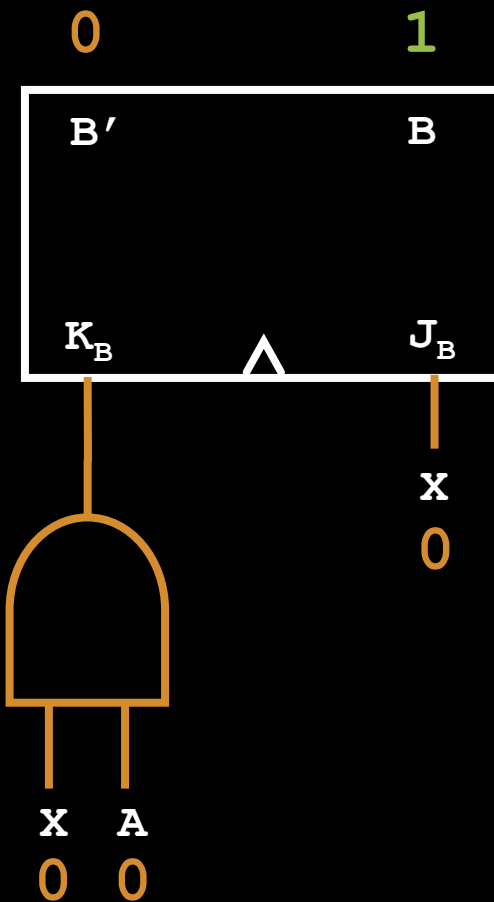
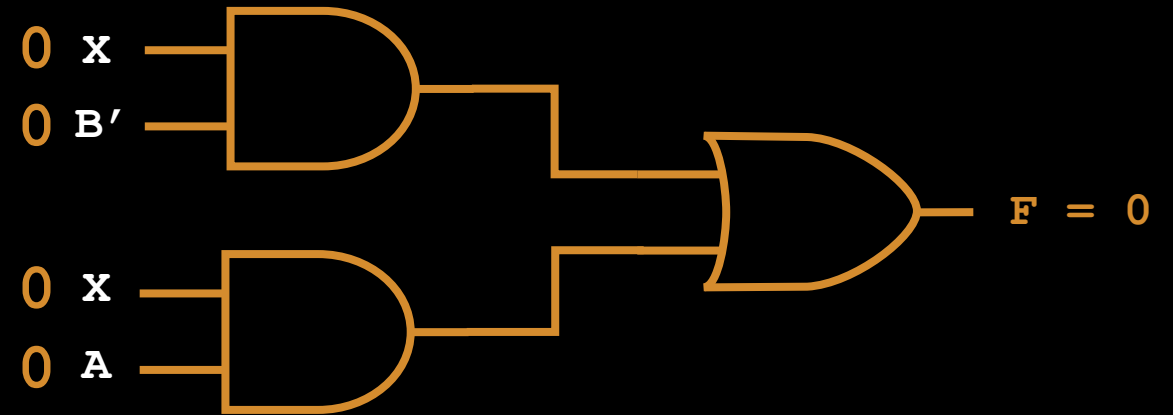
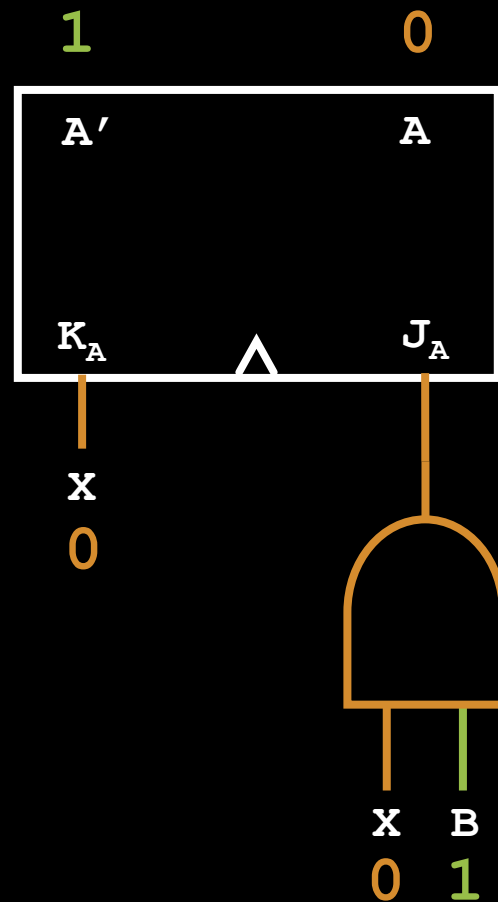


~~A.  $F = 0$~~

B.  $F = 1$

$X = \{1, 0, 1\}$

Cycle = 2

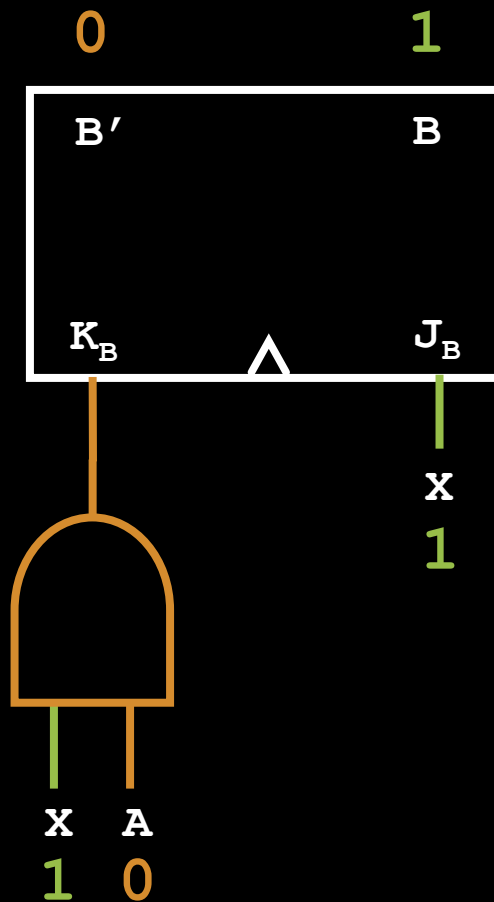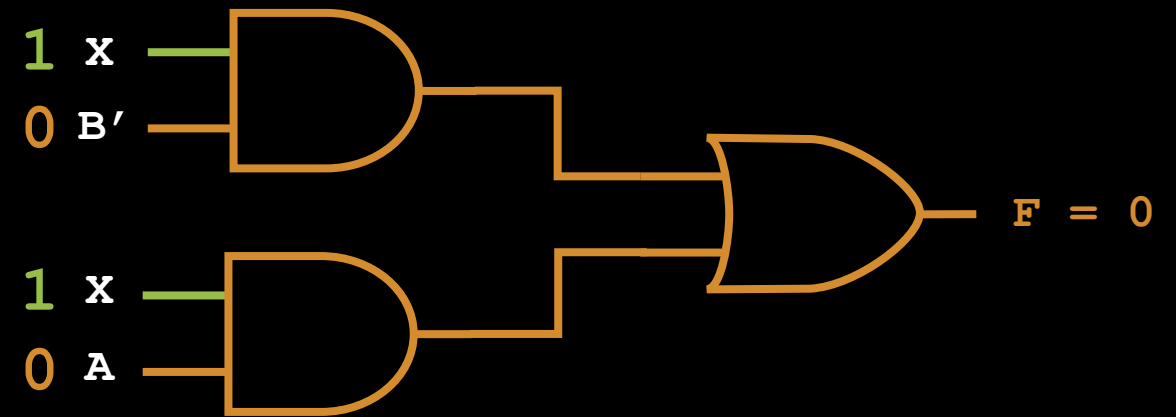
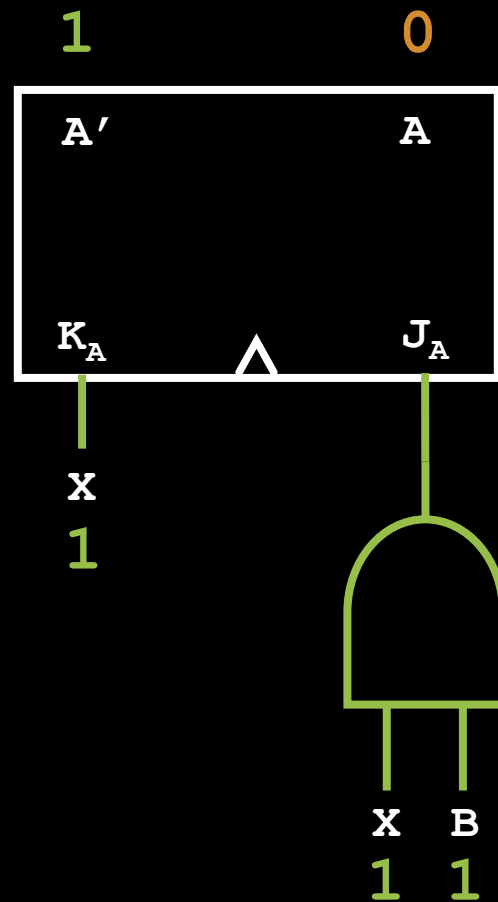


~~A.  $F = 0$~~

B.  $F = 1$

$X = \{0, 1\}$

Cycle = 3


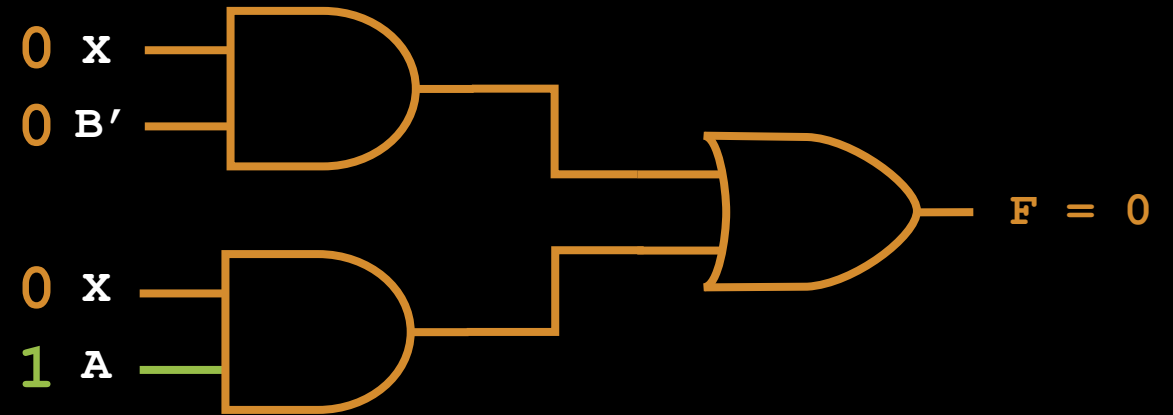
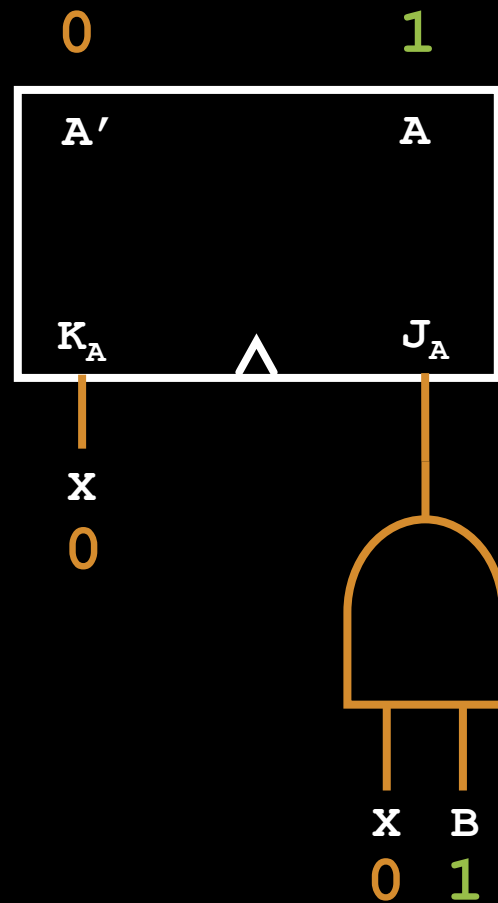


~~A.  $F = 0$~~

B.  $F = 1$

$X = \{1\}$

Cycle = 4

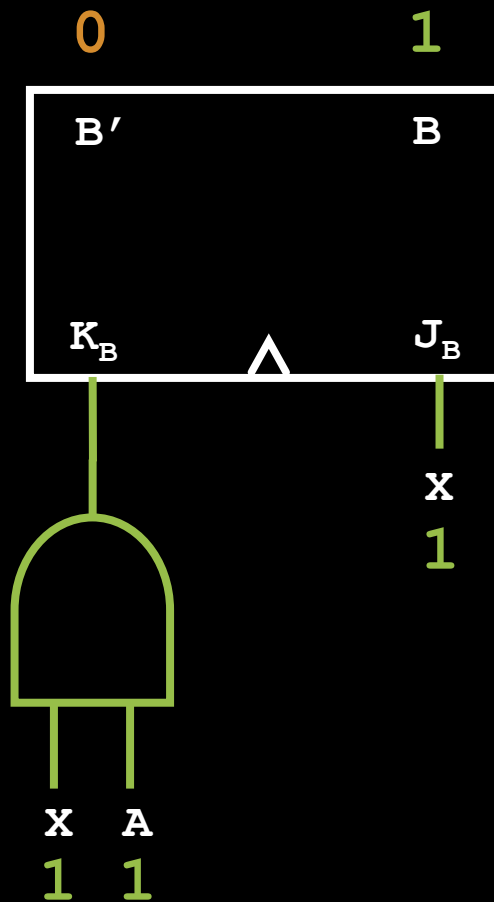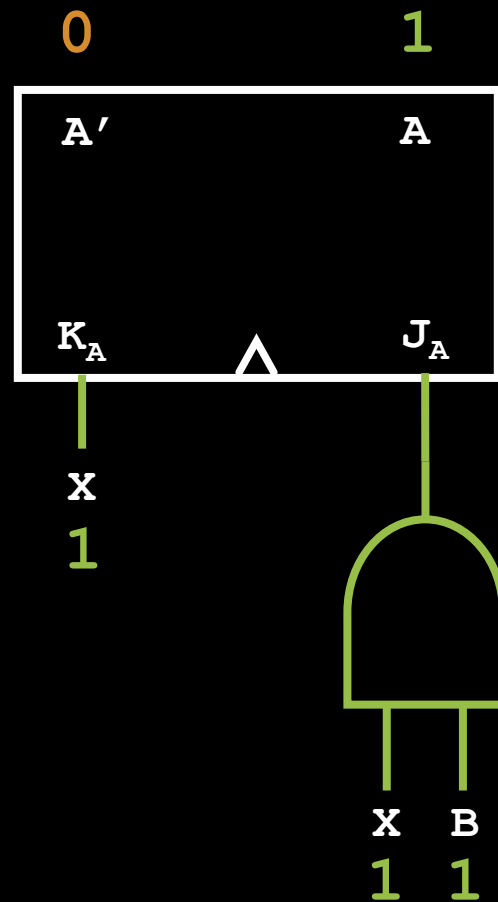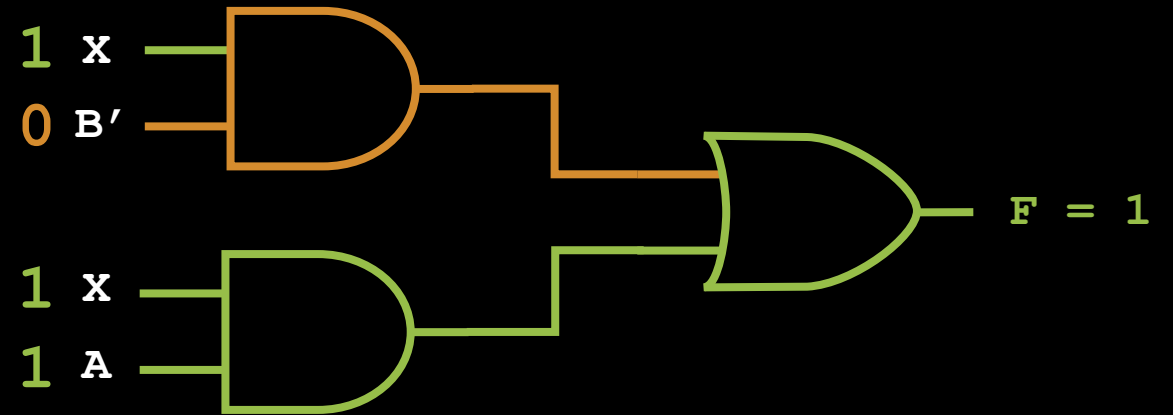





# Timing Charts

Sequential Circuit Analysis | Modern Digital System Design
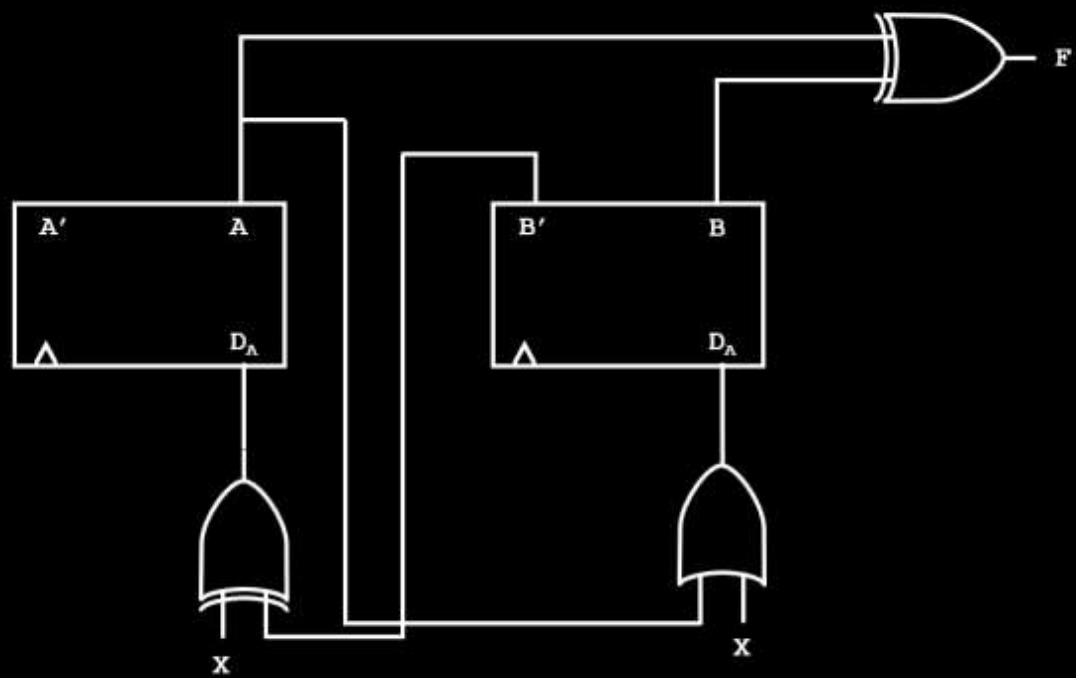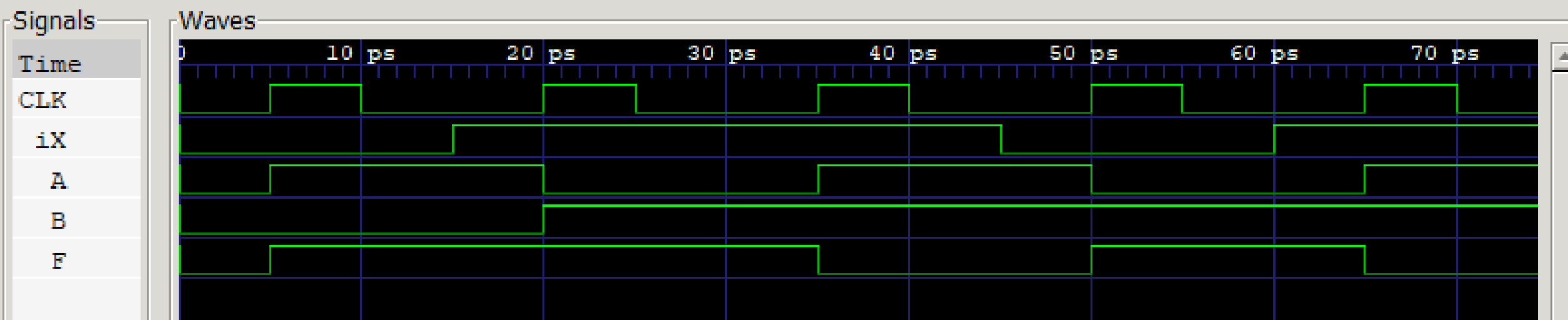
# Timing Charts

- We've already seen timing charts in our Verilog project.
- The **GTKWave** files that we view from our test benches are **timing charts**.









Signals

| Time    |
|---------|
| CLK = 0 |
| A = 0   |
| B = 0   |
| F = 1   |
| iX = 1  |

Waves

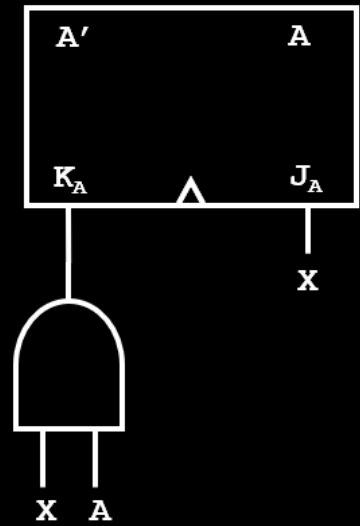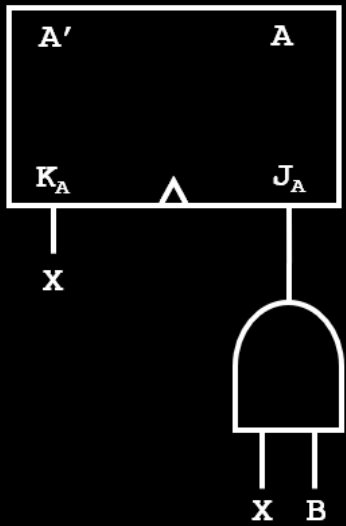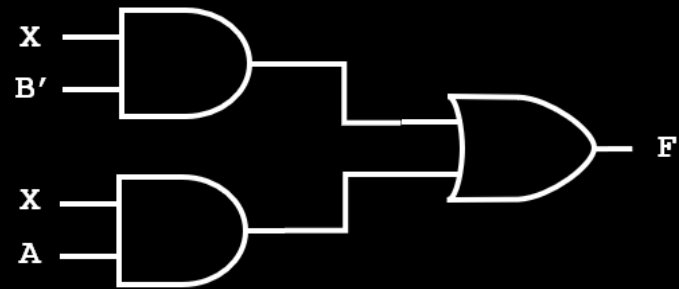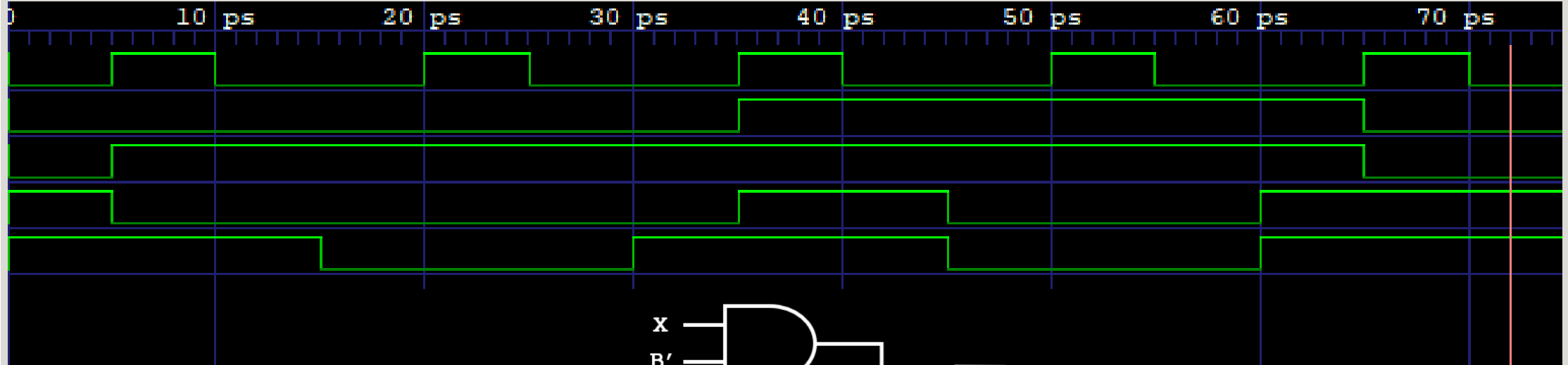

A large, light teal circle is positioned on the left side of the frame, partially overlapping a dark teal background. The circle is centered vertically and horizontally relative to the text it contains.

What questions do you  
have?

# EXAM QUESTION: Timing Charts


What is the input sequence,  $X$ , that is shown in the following timing chart?

A.  $X = \{1, 1, 0, 1, 0\}$

B.  $X = \{0, 1, 0, 1, 1\}$

C.  $X = \{1, 0, 0, 0, 1\}$

D.  $X = \{0, 1, 0, 0, 1\}$

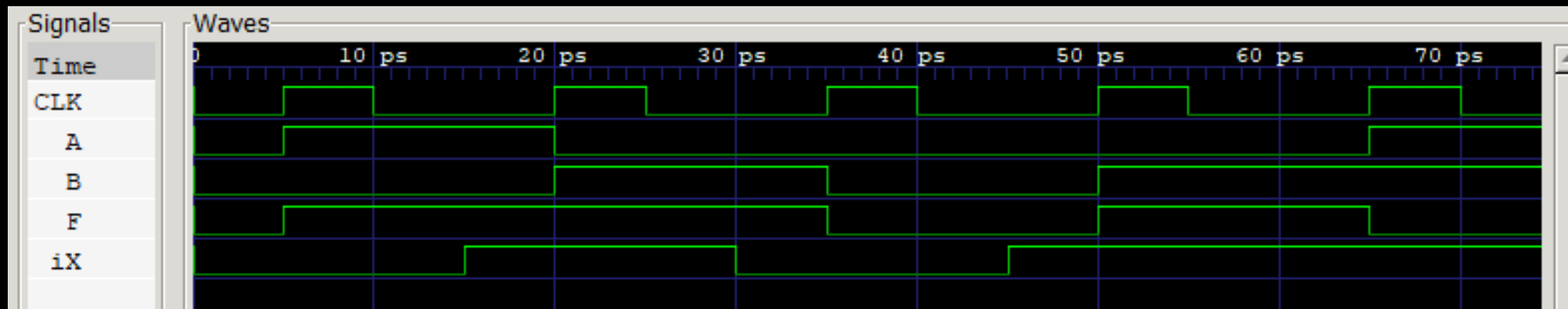

# EXAM QUESTION: Timing Charts


What is the input sequence, X, that is shown in the following timing chart?

~~A.  $X = \{1, 1, 0, 1, 0\}$~~

B.  $X = \{0, 1, 0, 1, 1\}$

~~C.  $X = \{1, 0, 0, 0, 1\}$~~

~~D.  $X = \{0, 1, 0, 0, 1\}$~~

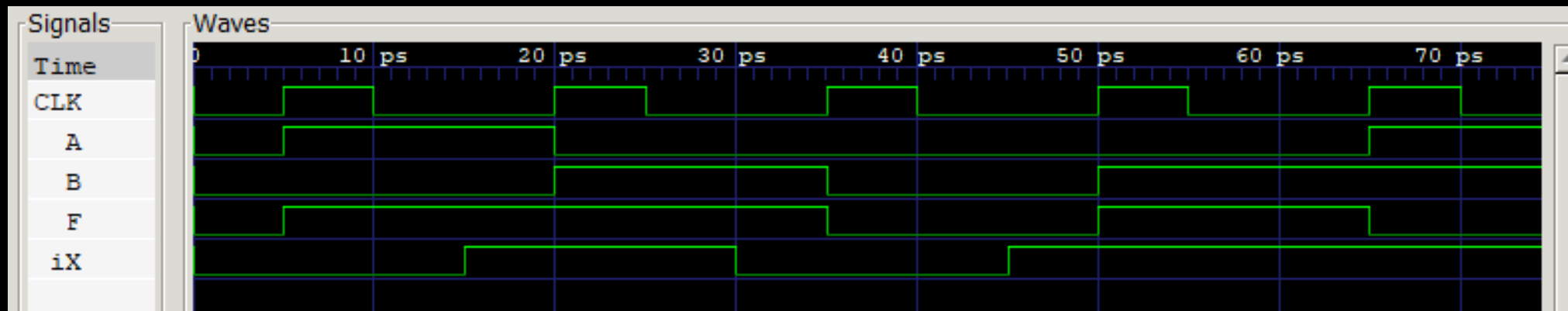



# ▼ Mealy versus Moore Machines

Analysis of Sequential Circuits | Modern Digital System Design


# Mealy versus Moore Machines

Sequential circuits are categorized into two types:

1. Moore Machines
2. Mealy Machines



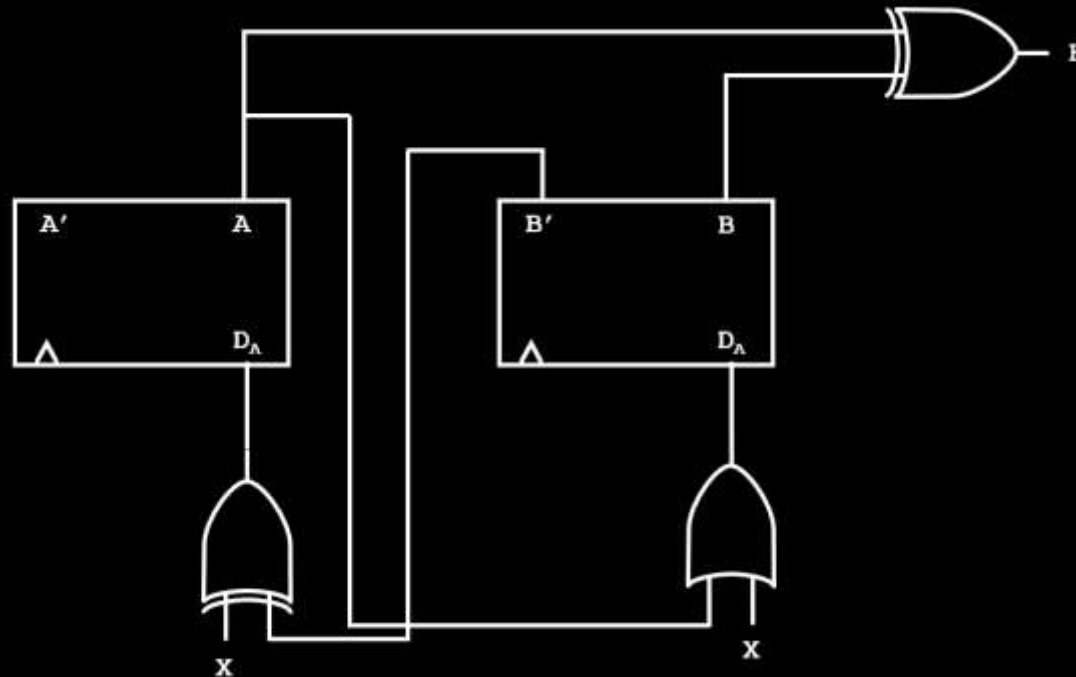
# Moore Machines

A **Moore Machine** is a sequential circuit in which the output is a function **only of the present state**.


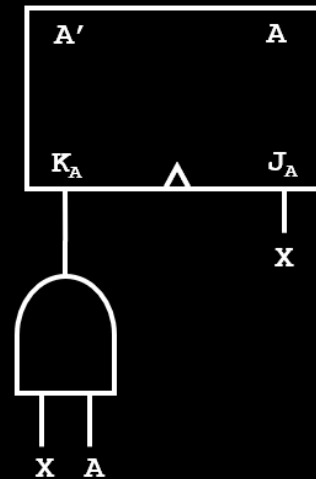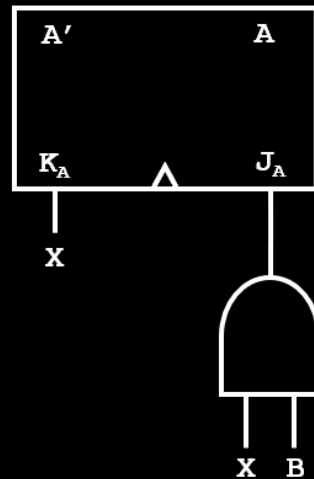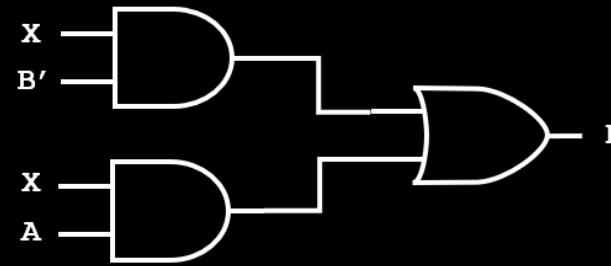
# Mealy Machine

A **Mealy Machine** is a sequential circuit in which the output is a function of **both the present state and the input**.






What questions do you  
have?



# EXAM QUESTION: Mealy vs. Moore Machines

Is the sequential circuit a Mealy Machine or a Moore Machine?

- A. Mealy Machine
- B. Moore Machine

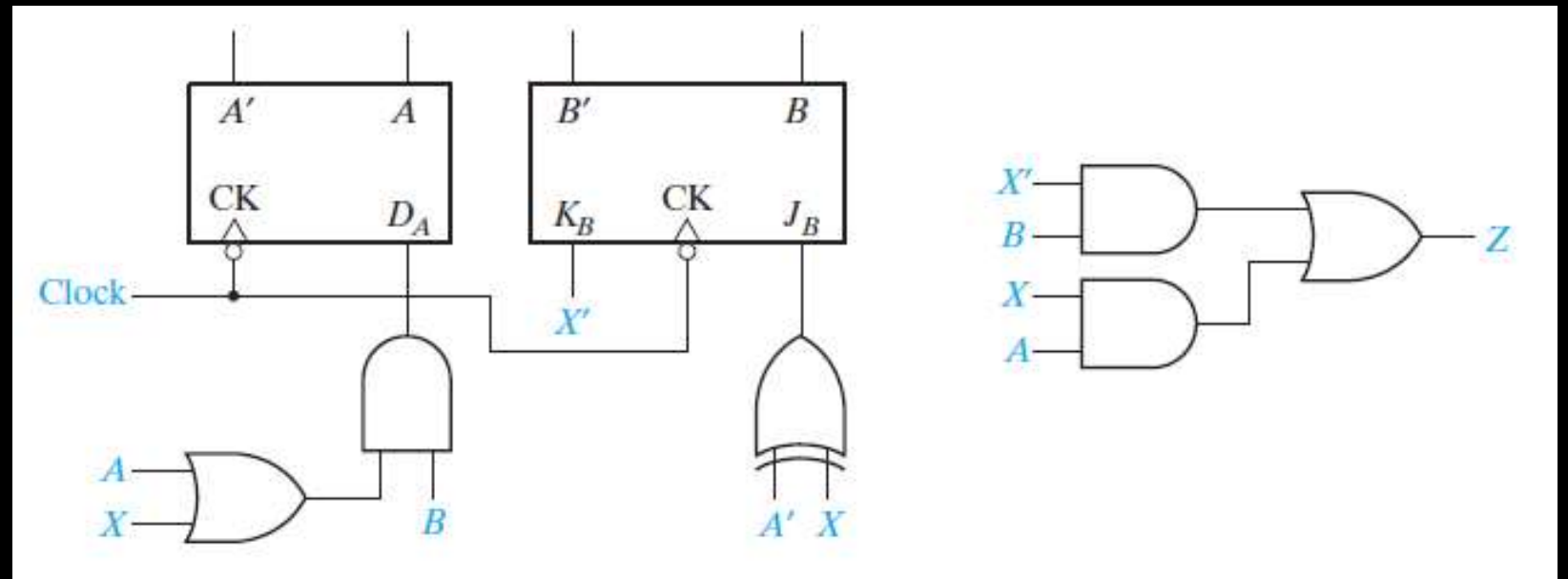


# EXAM QUESTION: Mealy vs. Moore Machines

Is the sequential circuit a Mealy Machine or a Moore Machine?

A. Mealy Machine

~~B. Moore Machine~~

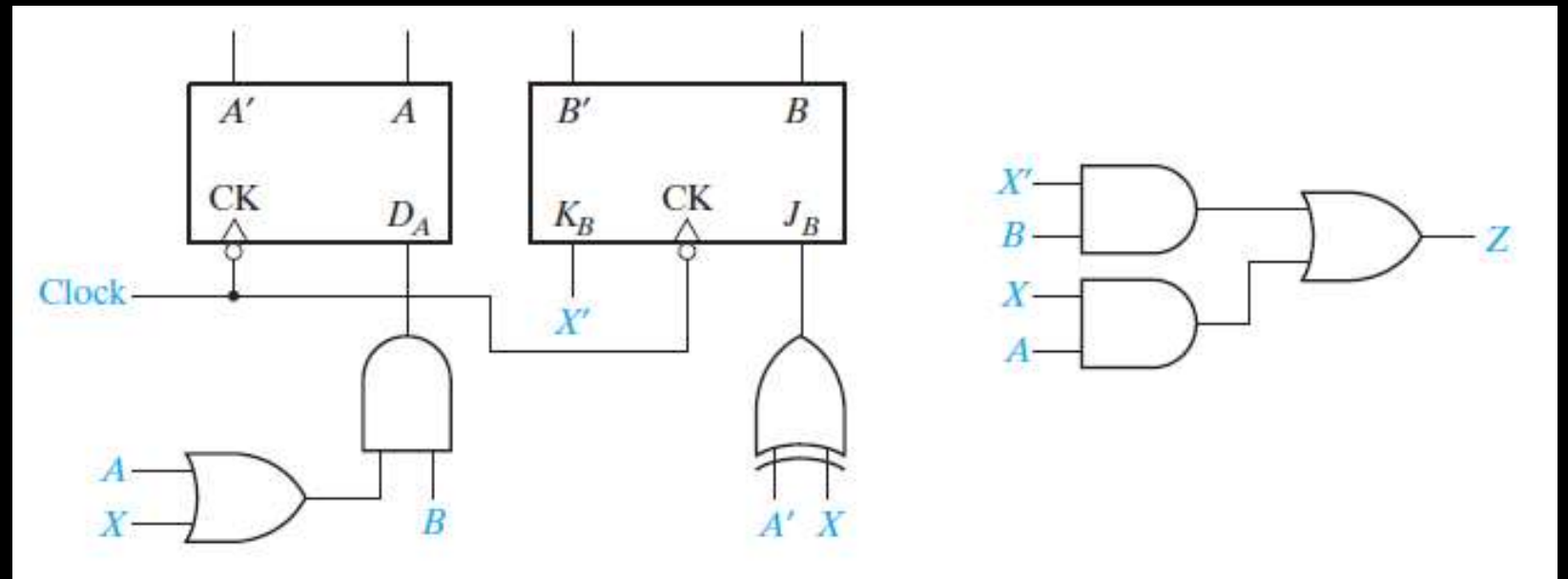

# Lecture Recap



Signal Tracing



Timing Charts



Mealy versus Moore Machines

What questions  
do you have?





# Sequential Circuit Analysis

ECE 2372 | Modern Digital System Design | Texas Tech University

