



Binary Counters

ECE 2372 | Modern Digital System Design | Texas Tech University

Lecture Overview

- Shift Registers
- Synchronous Binary Counters
- Counters for Other Sequences


Shift Registers

Binary Counters | Modern Digital System Design

Shift Registers: Definition


A **shift register** is a register in which binary data can be stored, and this data can be shifted to the left or right when a shift signal is applied.

Shift Registers: Right-Shift Register

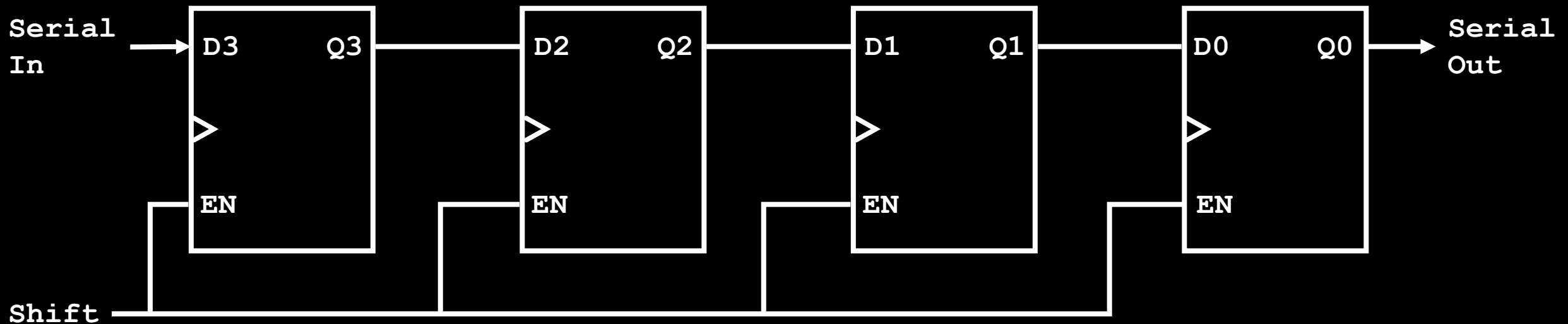

This type of Shift Register is also called a “Serial-in, Serial-out” shift register

 Shift Registers: Serial-In, Parallel-Out (SIPO)



Shift Registers: SIPO Example


Suppose a 4-bit SIPO register like the one on the previous slide. If all the flip-flops are initially at rest, `Shift` is held at 1, and the input bit-stream is,

$$SI = \{0, 1, 0, 1, 1, 0, 1\}$$

What will be the parallel output at the end of the 5th clock cycle?

$$P = \{1, 1, 0, 1\}$$

Shift Registers: SIPO Example

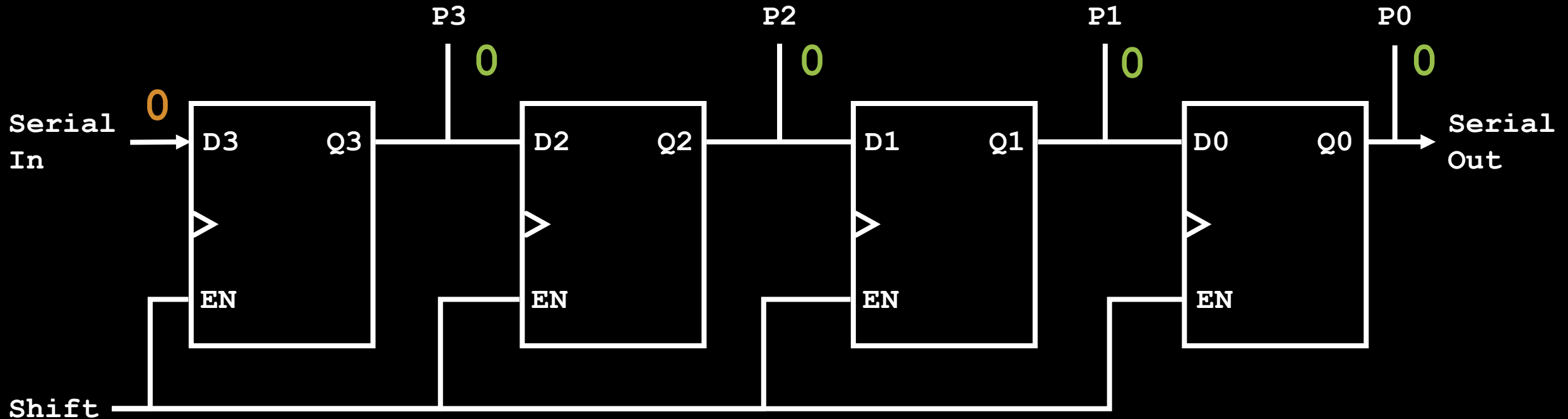


$SI = \{0, 1, 0, 1, 1, 0\}$

$P = \{0, 0, 0, 0\}$

$Cycle = 0$

Shift Registers: SIPO Example

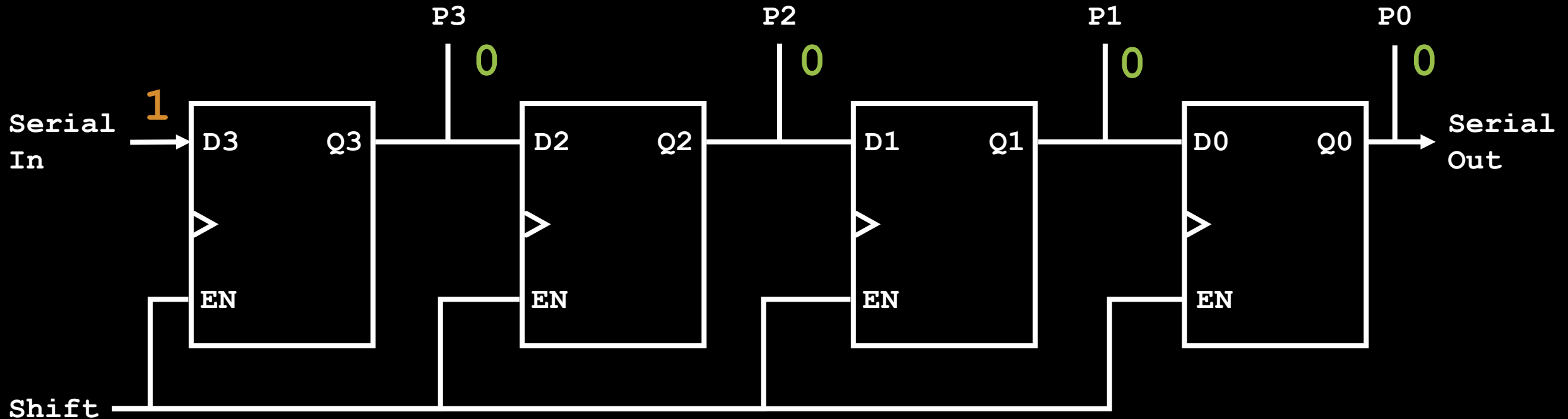


$SI = \{1, 0, 1, 1, 0\}$

$P = \{0, 0, 0, 0\}$

$Cycle = 1$

Shift Registers: SIPO Example

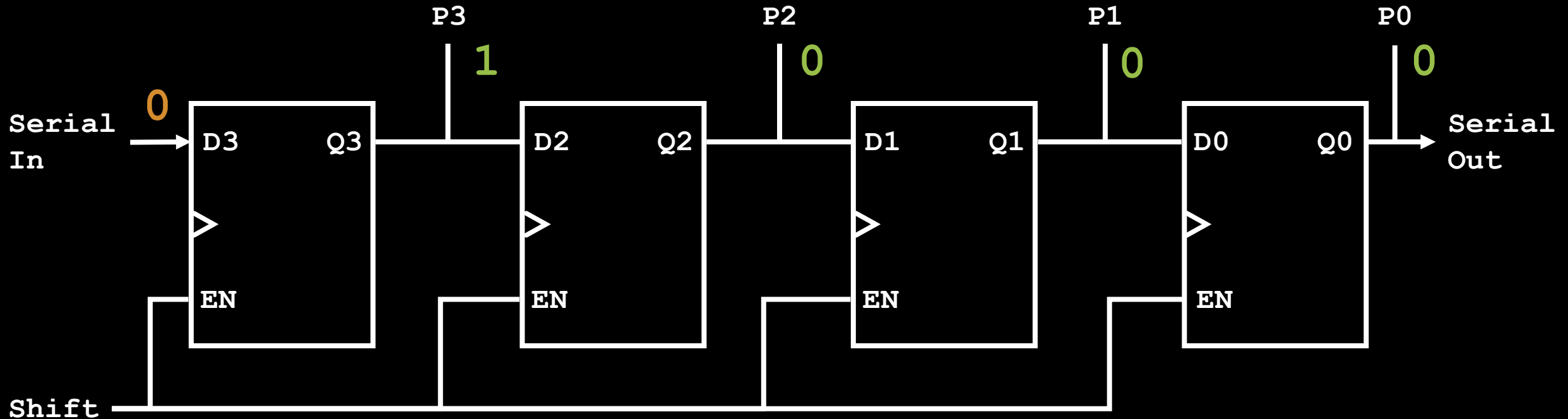


$SI = \{0, 1, 1, 0\}$

$P = \{1, 0, 0, 0\}$

$Cycle = 2$

Shift Registers: SIPO Example

 


$SI = \{1, 1, 0\}$

$P = \{0, 1, 0, 0\}$

$Cycle = 3$

Shift Registers: SIPO Example

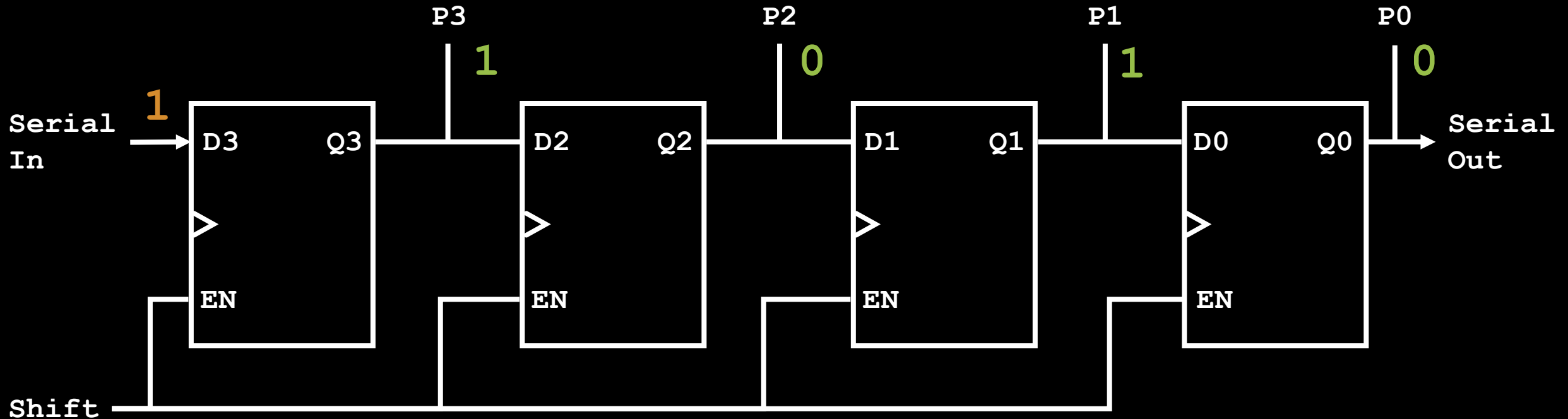


$SI = \{1, 0\}$

$P = \{1, 0, 1, 0\}$

$Cycle = 4$

Shift Registers: SIPO Example

 

$SI = \{0\}$

$P = \{1, 1, 0, 1\}$

$Cycle = 5$

Shift Registers: SIPO Example


Suppose a 4-bit SIPO register like the one on the previous slide. If all the flip-flops are initially at rest, `Shift` is held at 1, and the input bit-stream is,

$$SI = \{0, 1, 0, 1, 1, 0, 1\}$$


What will be the parallel output at the end of the 5th clock cycle?

$$P = \{1, 1, 0, 1\}$$

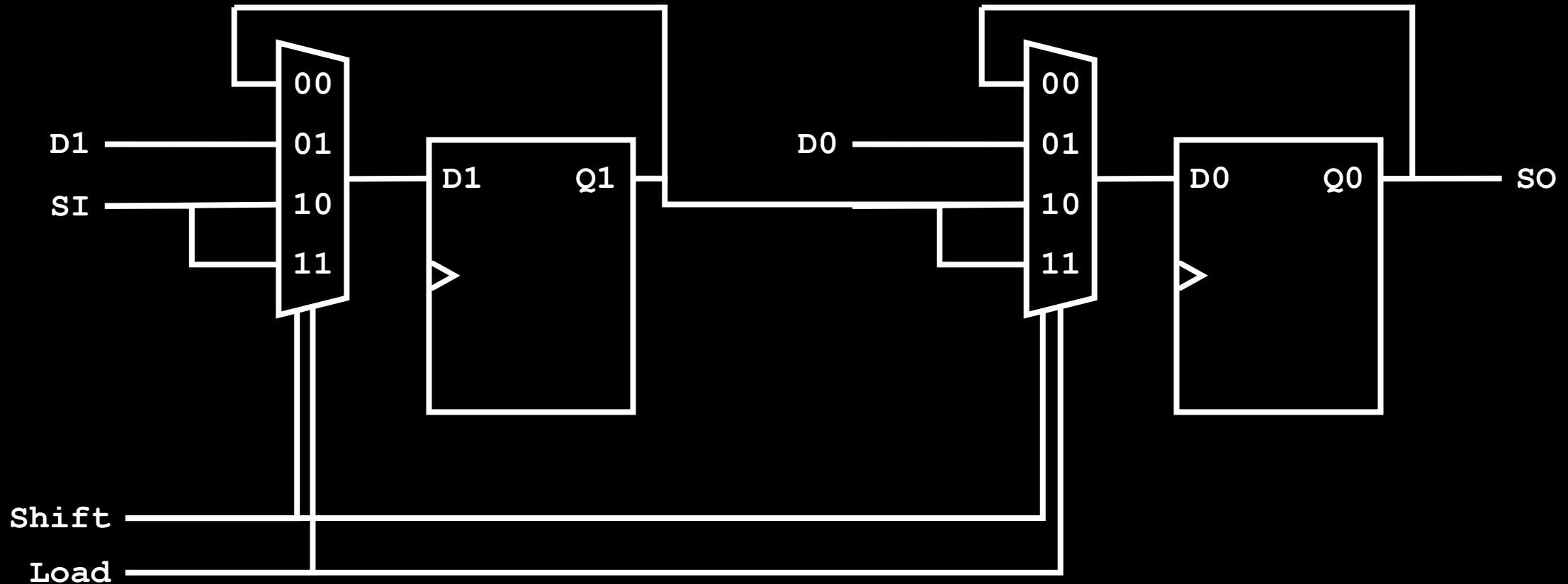Shift-Registers: Parallel-In, Parallel-Out (PIPO)



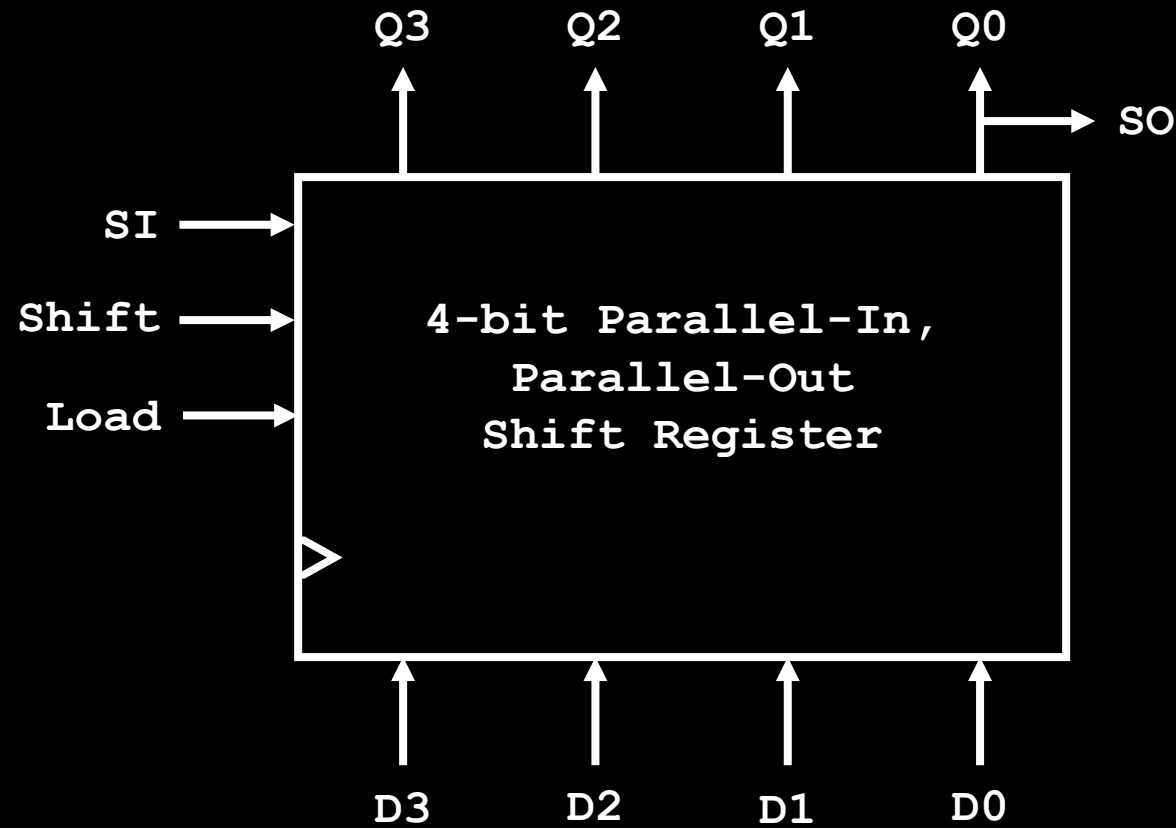Shift-Registers: Parallel-In, Parallel-Out (PIPO)



Shift Registers: Parallel-In, Parallel-Out (PIPO)

INPUTS		NEXT STATE				ACTION
Shift	Load	Q_3^+	Q_2^+	Q_1^+	Q_0^+	
0	0	Q_3	Q_2	Q_1	Q_0	NO CHANGE
0	1	D_3	D_2	D_1	D_0	LOAD
1	X	SI	Q_3	Q_2	Q_1	SHIFT RIGHT

+
◦ • What questions do you
have?

EXAM QUESTION: Shift Registers

A 4-bit PIPO right shift register is initially at rest. What will the output, Q, be at the end of the following sequence on inputs?

- A. $Q = \{1, 1, 1, 1\}$
- B. $Q = \{0, 0, 1, 1\}$
- C. $Q = \{1, 0, 1, 1\}$
- D. $Q = \{0, 1, 1, 1\}$

SI	Shift	Load	D
0	0	1	{0, 1, 0, 1}
0	0	0	{0, 1, 1, 0}
1	1	0	{0, 1, 1, 0}
1	1	0	{1, 0, 0, 1}
0	0	0	{1, 0, 1, 1}
1	1	1	{1, 1, 0, 1}
0	1	0	{1, 1, 1, 1}

EXAM QUESTION: Shift Registers

A 4-bit PIPO right shift register is initially at rest. What will the output, Q, be at the end of the following sequence on inputs?

~~A. $Q = \{1, 1, 1, 1\}$~~

~~B. $Q = \{0, 0, 1, 1\}$~~

~~C. $Q = \{1, 0, 1, 1\}$~~

D. $Q = \{0, 1, 1, 1\}$

SI	Shift	Load	D
0	0	1	{ 0, 1, 0, 1 }
0	0	0	{ 0, 1, 1, 0 }
1	1	0	{ 0, 1, 1, 0 }
1	1	0	{ 1, 0, 0, 1 }
0	0	0	{ 1, 0, 1, 1 }
1	1	1	{ 1, 1, 0, 1 }
0	1	0	{ 1, 1, 1, 1 }

$Q = \{0, 1, 0, 1\}$

$Q = \{0, 1, 0, 1\}$

$Q = \{1, 0, 1, 0\}$

$Q = \{1, 1, 0, 1\}$

$Q = \{1, 1, 0, 1\}$

$Q = \{1, 1, 1, 0\}$

$Q = \{0, 1, 1, 1\}$



Synchronous Binary Counters

Binary Counters | Modern Digital System Design

Synchronous Binary Counters

What if we wanted to apply this same concept of chaining flip-flops together to count through a predetermined sequence of binary values?

Synchronous Binary Counters

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

What do you notice about the relationship between A, B, and C that might be useful to us?

Synchronous Binary Counters


A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

What do you notice about the relationship between A, B, and C that might be useful to us?

Notice that every bit toggles when there is a falling edge on the bit to its right.

What flip-flop likes to toggle?

Synchronous Binary Counters

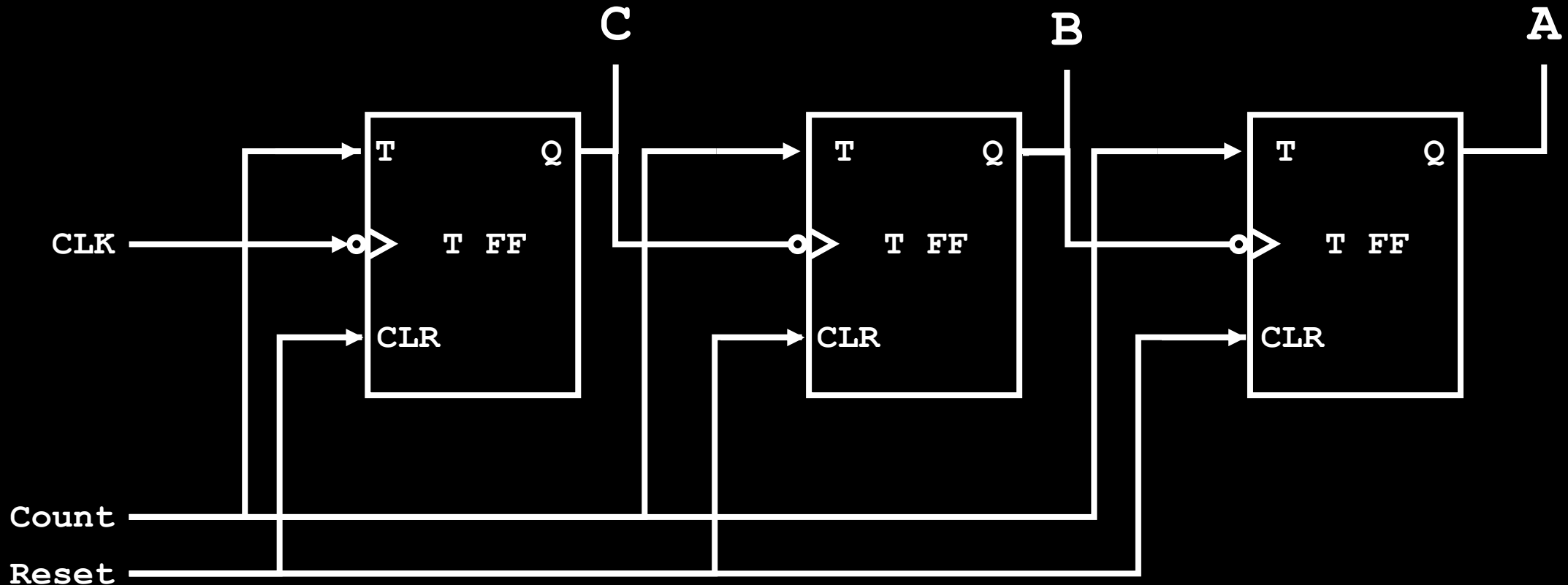

+
◦ • What questions do you
have?

EXAM QUESTION: Synchronous Binary Counter

A 4-bit synchronous binary counter is initially at rest. What will the state of the counter be at the end of the following sequence of inputs?

A. $\{A, B, C\} = 3'b111$

B. $\{A, B, C\} = 3'b100$

C. $\{A, B, C\} = 3'b101$

D. $\{A, B, C\} = 3'b110$

Count	Reset
1	0
1	1
1	0
1	0
0	0
1	0
1	0

EXAM QUESTION: Synchronous Binary Counter

A 4-bit synchronous binary counter is initially at rest. What will the state of the counter be at the end of the following sequence of inputs?

~~A. $\{A, B, C\} = 3'b111$~~

B. $\{A, B, C\} = 3'b100$

~~C. $\{A, B, C\} = 3'b101$~~

~~D. $\{A, B, C\} = 3'b110$~~

Count	Reset	
1	0	$\{A, B, C\} = 3'b001$
1	1	$\{A, B, C\} = 3'b000$
1	0	$\{A, B, C\} = 3'b001$
1	0	$\{A, B, C\} = 3'b010$
0	0	$\{A, B, C\} = 3'b010$
1	0	$\{A, B, C\} = 3'b011$
1	0	$\{A, B, C\} = 3'b100$

Counters for Other Sequences

Binary Counters | Modern Digital System Design

Counters for Other Sequences

- Usually, our binary counters will count in the traditional way.
- Sometimes, we want counters that can move through an arbitrary sequence.
- To do this, we'll need to apply some combinational logic design.

Counters for Other Sequences

Let's design a 3-bit gray code counter

Q_A	Q_B	Q_C
0	0	0
0	0	1
0	1	1
0	1	0
1	1	0
1	1	1
1	0	1
1	0	0

<i>Count</i>	Q_A	Q_B	Q_C	Q_A^+	Q_B^+	Q_C^+
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	1	0	0
0	1	0	1	1	0	1
0	1	1	0	1	1	0
0	1	1	1	1	1	1
1	0	0	0	0	0	1
1	0	0	1	0	1	1
1	0	1	0	1	1	0
1	0	1	1	0	1	0
1	1	0	0	0	0	0
1	1	0	1	1	0	0
1	1	1	0	1	1	1
1	1	1	1	1	0	1

$$Q_A^+(Count, Q_A, Q_B, Q_C) = \sum_m (4, 5, 6, 7, 10, 13, 14, 15)$$

$$Q_B^+(Count, Q_A, Q_B, Q_C) = \sum_m (2, 3, 6, 7, 9, 10, 11, 14)$$

$$Q_C^+(Count, Q_A, Q_B, Q_C) = \sum_m (1, 3, 5, 7, 8, 9, 14, 15)$$

		$Q_{B'}$		Q_B		
Count'	Q_A^+	0 0	0 1	0 3	0 2	$Q_{A'}$
		1 4	1 5	1 7	1 6	
Count		0 12	1 13	1 15	1 14	Q_A
		0 8	0 9	0 11	1 10	$Q_{A'}$
		$Q_{C'}$	Q_C	$Q_{C'}$		

Q_A^+

	Q_B'		Q_B	
Count'	0 0	0 1	0 3	0 2
	1 4	1 5	1 7	1 6
Count	0 12	1 13	1 15	1 14
	0 8	0 9	0 11	1 10
	Q_C'	Q_C	Q_C'	


Q_A'
 Q_A
 Q_A'

$$Q_A^+ = \text{Count}' Q_A +$$

Q_A^+

	Q_B'		Q_B		
	0	0	0	0	Q_A'
Count'	0	1	3	2	
	1	1	1	1	
	4	5	7	6	Q_A
Count	0	1	1	1	
	12	13	15	14	
	0	0	0	1	Q_A'
	8	9	11	10	
	Q_C'	Q_C	Q_C'		
 
$$Q_A^+ = \text{Count}' Q_A + Q_A Q_C +$$



$$Q_A^+ = \text{Count}' Q_A + Q_A Q_C + Q_A Q_B +$$

Q_A^+

	Q_B'		Q_B	
	0	0	0	0
	0	1	3	2
Count'	1	1	1	1
	4	5	7	6
	0	1	1	1
Count	12	13	15	14
	0	0	0	1
	8	9	11	10
	Q_C'	Q_C	Q_C'	

Q_A'

Q_A

Q_A'

$$Q_A^+ = \text{Count}' Q_A + Q_A Q_C + Q_A Q_B + \text{Count} Q_B Q_C'$$

Solving the other K-maps yields,

$$Q_A^+ = \textit{Count}' Q_A + Q_A Q_C + Q_A Q_B + \textit{Count} Q_B Q_C'$$

$$Q_B^+ = Q_B Q_C' + \textit{Count}' Q_B + \textit{Count} Q_A' Q_C$$

$$Q_C^+ = \textit{Count}' Q_C + \textit{Count} Q_A Q_B + \textit{Count} Q_A' Q_B'$$

```

8  module gray_count(Count, CLK, Q);
9      // CONTROL INPUTS
10     input Count, CLK;
11
12     // Data Outputs
13     output [2:0] Q;
14
15     // Internal Registers
16     reg qA = 1'b0;
17     reg qB = 1'b0;
18     reg qC = 1'b0;
19
20     // RTL Logic Implementation
21     always @(posedge CLK) begin
22         qA <= ~Count & qA | qA & qC | qA & qB | Count & qB & ~qC;
23         qB <= qB & ~qC | ~Count & qB | Count & ~qA & qC;
24         qC <= ~Count & qC | Count & qA & qB | Count & ~qA & ~qB;
25     end
26
27     // Combinational Logic Implementation
28     assign Q = {qA, qB, qC};
29
30 endmodule

```



```
PS C:\Users\derek\Desktop\ece2372_305_example> iverilog -o gray_count.vvp gray_count_test.v
```

```
PS C:\Users\derek\Desktop\ece2372_305_example> vvp gray_count.vvp
```

```
Start of test bench for 3-bit gray code counter.
```

```
VCD info: dumpfile gray_count.vcd opened for output.
```

```
Count = 0, Q = 000
```

```
Count = 0, Q = 000
```

```
Count = 0, Q = 000
```

```
Count = 0, Q = 000
```

```
Count = 1, Q = 001
```

```
Count = 1, Q = 011
```

```
Count = 1, Q = 010
```

```
Count = 1, Q = 110
```

```
Count = 1, Q = 111
```

```
Count = 1, Q = 101
```

```
Count = 1, Q = 100
```

```
Count = 1, Q = 000
```

```
Count = 1, Q = 001
```

```
Count = 1, Q = 011
```

```
Count = 1, Q = 010
```


```
Count = 0, Q = 110
```

```
Count = 0, Q = 110
```

```
Count = 0, Q = 110
```

```
Count = 0, Q = 110
```

```
End of test bench.
```

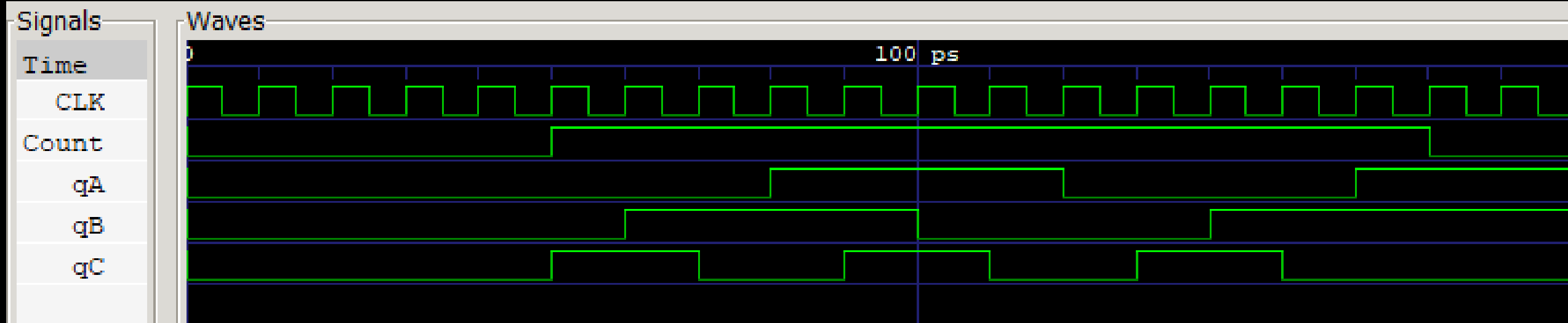

+
◦ • What questions do you
have?

EXAM QUESTION: Arbitrary Binary Counters

What is the next-state equation for flip-flop A in a 2-bit arbitrary sequence binary counter with the given sequence?

A. $Q_A^+ = \text{Count}'Q_A + Q_A'Q_B' + \text{Count}'Q_AQ_B$

B. $Q_A^+ = Q_AQ_B + \text{Count}'Q_A'Q_B' + \text{Count}Q_AQ_B$

C. $Q_A^+ = \text{Count}'Q_A + Q_AQ_B + \text{Count}Q_A'Q_B'$

D. $Q_A^+ = \text{Count}'Q_A' + Q_A'Q_B + \text{Count}Q_AQ_B'$

Q_A^+	Q_B^+
1	1
1	0
0	1
0	0

EXAM QUESTION: Arbitrary Binary Counters

What is the next-state equation for flip-flop A in a 2-bit arbitrary sequence binary counter with the given sequence?

~~A. $Q_A^+ = \text{Count}'Q_A + Q_AQ_B' + \text{Count}'Q_AQ_B$~~

~~B. $Q_A^+ = Q_AQ_B + \text{Count}'Q_AQ_B' + \text{Count}Q_AQ_B$~~

C. $Q_A^+ = \text{Count}'Q_A + Q_AQ_B + \text{Count}Q_A'Q_B'$

~~D. $Q_A^+ = \text{Count}'Q_A' + Q_A'Q_B + \text{Count}Q_AQ_B'$~~

Q_A^+	Q_B^+
1	1
1	0
0	1
0	0

Q_A^+	Q_B^+
1	1
1	0
0	1
0	0

<i>Count</i>	Q_A	Q_B	Q_A^+	Q_B^+
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	1	1
1	0	1	0	0
1	1	0	0	1
1	1	1	1	0

$$Q_A^+(Count, Q_A, Q_B) = \sum_m (2, 3, 4, 7)$$

$$Q_A^+(Count, Q_A, Q_B) = \sum_m (2, 3, 4, 7)$$

		Q_A'		Q_A	
Q_A^+	Count'	0 0	0 1	1 3	1 2
	Count	1 4	0 5	1 7	0 6
		Q_B'	Q_B		Q_B'

	Q_A^+		Q_A'		Q_A	
Count'	0 0	0 1	1 3	1 2		
Count	1 4	0 5	1 7	0 6		
	Q_B'		Q_B		Q_B'	

$$Q_A^+(Count, Q_A, Q_B) = \text{Count}' Q_A +$$

Q_A^+

	Q_A'		Q_A	
Count'	0 0	0 1	1 3	1 2
Count	1 4	0 5	1 7	0 6
	Q_B'	Q_B	Q_B'	

$$Q_A^+(Count, Q_A, Q_B) = \text{Count}' Q_A + Q_A Q_B +$$

Q_A^+

	Q_A'		Q_A	
Count'	0 0	0 1	1 3	1 2
Count	1 4	0 5	1 7	0 6
	Q_B'	Q_B	Q_B'	

$$Q_A^+(Count, Q_A, Q_B) = \text{Count}'Q_A + Q_AQ_B + \text{Count}Q_A'Q_B'$$

EXAM QUESTION: Arbitrary Binary Counters

What is the next-state equation for flip-flop A in a 2-bit arbitrary sequence binary counter with the given sequence?

~~A. $Q_A^+ = \text{Count}'Q_A + Q_AQ_B' + \text{Count}'Q_AQ_B$~~

~~B. $Q_A^+ = Q_AQ_B + \text{Count}'Q_AQ_B' + \text{Count}Q_AQ_B$~~

C. $Q_A^+ = \text{Count}'Q_A + Q_AQ_B + \text{Count}Q_A'Q_B'$

~~D. $Q_A^+ = \text{Count}'Q_A' + Q_A'Q_B + \text{Count}Q_AQ_B'$~~

Q_A^+	Q_B^+
1	1
1	0
0	1
0	0

$$Q_A^+(\text{Count}, Q_A, Q_B) = \text{Count}'Q_A + Q_AQ_B + \text{Count}Q_A'Q_B'$$

Lecture Recap

- Shift Registers
- Synchronous Binary Counters
- Counters for Other Sequences

+
◦ • What questions do you
have?



Binary Counters

ECE 2372 | Modern Digital System Design | Texas Tech University