 




Register Transfer Level Programming

ECE 2372 Modern Digital System Design | Texas Tech University



Lecture Overview

- What is Register Transfer Level?
- RTL Syntax in Verilog HDL
- RTL Examples

What is Register Transfer Level?

Register Transfer Level Programming | Modern Digital System Design

What is Register Transfer Level?

- Register Transfer Level (RTL) is a design abstraction which models the flow of digital signals between registers and the logical operations performed on those signals.
- Most digital systems are designed at the RTL level.

```

8  module ff_d(D, CLK, Q);
9
10     // DATA INPUTS
11     input D;
12
13     // CONTROL INPUTS
14     input CLK;
15
16     // OUTPUT REGISTERS
17     output reg Q;
18
19     // RTL CIRCUIT IMPLEMENTATION
20     always @(posedge CLK)
21     begin
22         Q <= D;
23     end
24
25 endmodule

```

What is Register Transfer Level?

- RTL programming is very similar to computer programming.
- Similar structures are used
 - If/else
 - Loops
- Verilog is still not a programming language.
- It is common for new engineers to try and use RTL like C/C++.



What questions do you have?

EXAM QUESTION: Register Transfer Level

Which of the following RTL commands defines a 6-bit output register?

A. `reg[5:0] myReg;`

B. `output [5:0] myReg;`

C. `output reg [5:0] myReg;`

D. `output reg [6:0] myReg;`

EXAM QUESTION: Register Transfer Level

Which of the following RTL commands defines a 6-bit output register?

~~A. `reg[5:0] myReg;`~~

~~B. `output [5:0] myReg;`~~

C. `output reg [5:0] myReg;`

~~D. `output reg [6:0] myReg;`~~

RTL Syntax in Verilog HDL

Register Transfer Level Programming | Modern Digital System Design

RTL Syntax in Verilog HDL

- Registers
- Trigger
- If/Else Syntax in Verilog
- For Loops in Verilog
- While Loops in Verilog
- Non-blocking Assignment

RTL Syntax: Registers

- Registers are provided in Verilog HDL.
- Usually (but not always), you'll declare your output ports as registers.

16

17

```
// OUTPUT REGISTERS  
output reg Q;
```

RTL Syntax: Registers

- Registers can be declared to be N-bit long.

```
30  output reg [7:0] Accumulator;
```

RTL Syntax: Trigger

Register transfers are triggered using the `always@` command.

```
// RTL CIRCUIT IMPLEMENTATION
always @(posedge CLK)
begin
    Q <= D;
end
```

RTL Syntax: Trigger

```
27  always@(posedge CLK) // Rising Edge of CLK
28
29  always@(negedge CLK) // Falling Edge of CLK
30
31  always@(CLK) // Rising and Falling Edge of CLK
32
33  always@(*) // Any Rising or Falling Edge of ANY Input.
```

RTL Syntax: IF/ELSE

```
27  if (CONDITION)
28  begin
29  |    // EXECUTE IF TRUE
30  end
31  else
32  begin
33  |    // EXECUTE IF FALSE
34  end
```


RTL Syntax: FOR Loop

```
27   for (START; END_CONDITION; CHANGE)
28   begin
29       |    // EXECUTE
30   end
```

RTL Syntax: WHILE Loop

- While loops aren't commonly used, but they are available.

```
27  while (CONDITION)
28  begin
29      // EXECUTE WHILE CONDITION
30      // IS TRUE
31  end
```

Blocking vs Nonblocking Assignment

Verilog supports two separate types of assignment.

- **Blocking** – Will hold all execution until complete (synchronous)
- **Nonblocking** – Will not hold up execution (asynchronous)

```
27    // Nonblocking assignment
28    Q = D;
29
30    // Blocking Assignment
31    Q <= D;
```

RTL Syntax in Verilog HDL

- Registers
- Trigger
- If/Else Syntax in Verilog
- For Loops in Verilog
- While Loops in Verilog
- Non-blocking Assignment



What questions do you have?

EXAM QUESTION: RTL Syntax

Which of the following RTL commands will cause the logic instructions to trigger on the falling edge of CLK?

A. `always@ (posedge CLK) ;`

B. `always@ (negedge CLK) ;`

C. `always@ (CLK) ;`

D. `always@ (*) ;`

EXAM QUESTION: RTL Syntax

Which of the following RTL commands will cause the logic instructions to trigger on the falling edge of CLK?

~~A. always@(posedge CLK);~~

B. always@(negedge CLK);


~~C. always@(CLK);~~

~~D. always@(*);~~

RTL Examples

Register Transfer Level Programming | Modern Digital System Design

RTL Example: J-K Flip-Flop

 

Input	Output
$J = K = 0$	No Change
$J = 1, K = 0$	SET (After CLK Edge)
$J = 0, K = 1$	RESET (After CLK Edge)
$J = K = 1$	TOGGLE (After CLK Edge)

```

8  module ff_jk(J, K, CLK, Q);
9      // DATA INPUTS
10     input J, K;
11
12     // CONTROL INPUTS
13     input CLK;
14     // OUTPUT REGISTERS
15     output reg Q = 1'b0;
16
17     // RTL LOGIC IMPLEMENTATION
18     always @(posedge CLK)
19     begin
20         Q <= J & ~Q | ~K & Q;
21     end
22
23 endmodule

```

Test Benches in RTL

There are only two main things that are different about running a test bench on an RTL module.

1. Setup the clock
2. Manually stop the test.


Setup the Clock

```
// CLOCK
reg CLK = 1'b0;
always
begin
    CLK = ~CLK;
    #5;
end
```


Manually stop the test.

- If you don't stop the test manually, the clock will keep the test running forever.
- Stop the test with the `$finish` command.
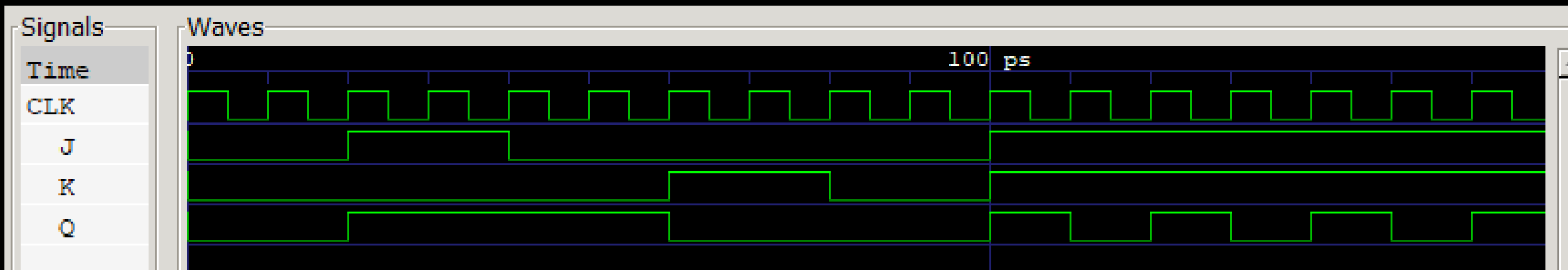
```
// TEST EXECUTION
initial begin
    $dumpfile("ff_jk.vcd");
    $dumpvars(0, ff_jk_test);
    {J, K} = 2'b00; #20;
    {J, K} = 2'b10; #20;
    {J, K} = 2'b00; #20;
    {J, K} = 2'b01; #20;
    {J, K} = 2'b00; #20;
    {J, K} = 2'b11; #20;
    #50;
    $finish;
end
```



RTL Example: Register Transfer

 


```
9  module reg_tran(D, S, ADDR, CLK, Q);
10      // DATA INPUTS
11      input [1:0] D;
12      // CONTROL INPUTS
13      input S, ADDR, CLK;
14      // DATA OUTPUTS
15      output [1:0] Q;
16      // INTERNAL REGISTERS
17      reg rA, rB, rX, rY;
```

```

19 // RTL LOGIC IMPLEMENTATION
20 always@(posedge CLK) begin
21     rA <= D[1];
22     rB <= D[0];
23
24     if(S == 0) begin
25         if (ADDR == 1) begin
26             rX <= rA;
27         end else begin
28             rY <= rA;
29         end
30     end else begin
31         if (ADDR == 1) begin
32             rX <= rB;
33         end else begin
34             rY <= rB;
35         end
36     end
37 end

```

```

39 // COMBINATIONAL LOGIC IMPLEMENTATION
40 assign Q[1] = rX;
41 assign Q[0] = rY;

```

RTL Examples: ALU Project

RTL Syntax drastically simplifies the implementation from the ALU project.

```
9      // DATA INPUTS
10     input [7:0] A, B;
11
12     // CONTROL INPUTS
13     input S, E;
14
15     // OUTPUT REGISTERS
16     output reg [7:0] W;
17
```

```
18      // RTL LOGIC IMPLEMENTATION
19      always@(*) begin
20          if (E == 1) begin
21              if (S == 0) begin
22                  W <= A + B;
23              end else begin
24                  W <= A - B;
25              end
26          end else begin
27              W <= 0;
28          end
29      end
```



What questions do you have?

Lecture Recap

- What is Register Transfer Level?
- RTL Syntax in Verilog HDL
- RTL Examples



What questions do you have?



Register Transfer Level Programming

ECE 2372 Modern Digital System Design | Texas Tech University

